

Schematic Creation and Transient Simulation


Author: Jinhua Wang

This tutorial will guide you to build an inverter step by step.


1. Open Cadence Virtuoso 6.1.6 in **ECE Guacamole**
2. Open **Library Manager**
3. Create a new library (e.g.: ECE 4220)

Note: If you are not sure how to do 1, 2 and 3, please refer to “**00_ Environment_Setup**”

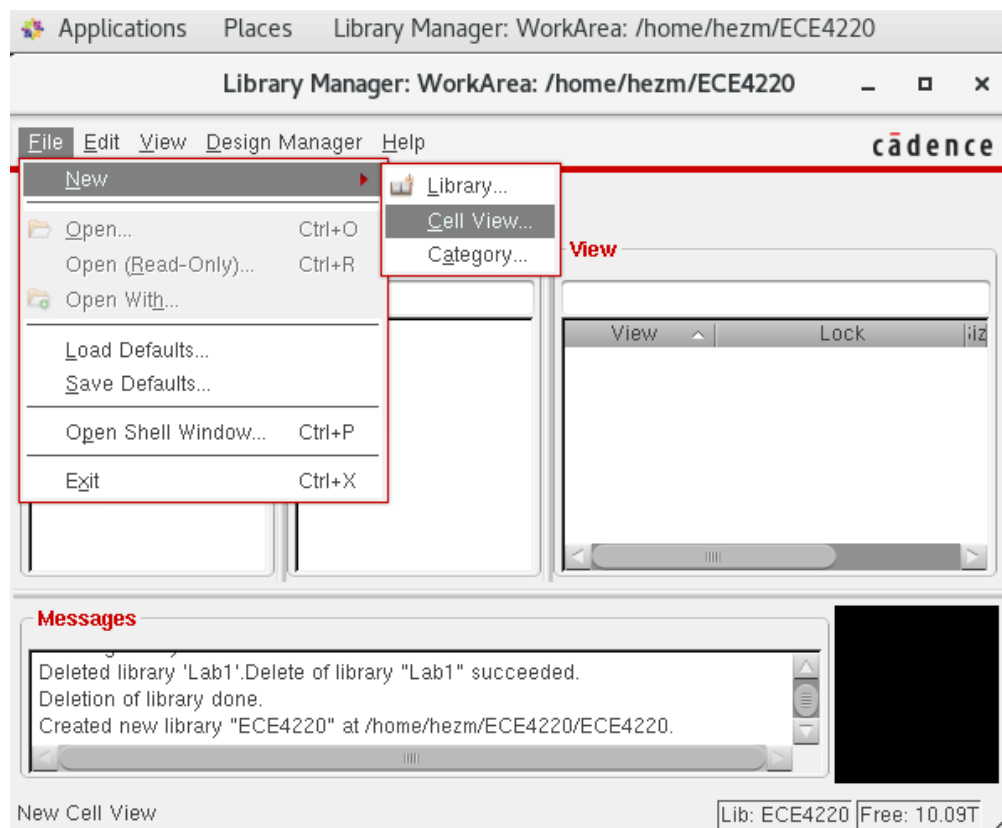
4. Under the library you just create, create a new cell view
 - a. Click **ECE4220** under **Library**
 - b. Click **File** in the tool bar on the top of the **Library Manager** window
 - c. Click **New** and then click **Cell View**



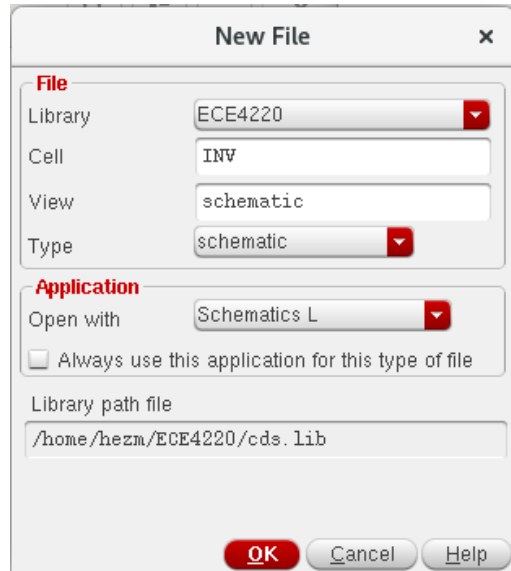
- d. A **New File** window pops up,
 - i. For **Cell**, give a name your cell (e.g. **INV**)
 - ii. For **View**, set it to **schematic**
 - iii. For **Type**, set it to **schematic**
 - iv. For **Open with**, set it to **Schematic L** and click **OK**



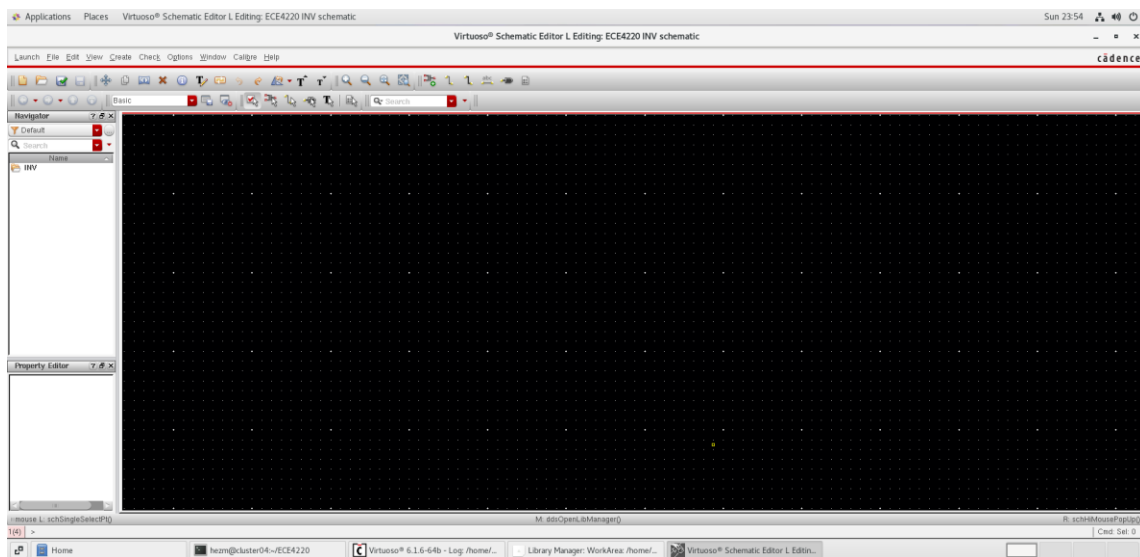e. An empty schematic editor window should pop up



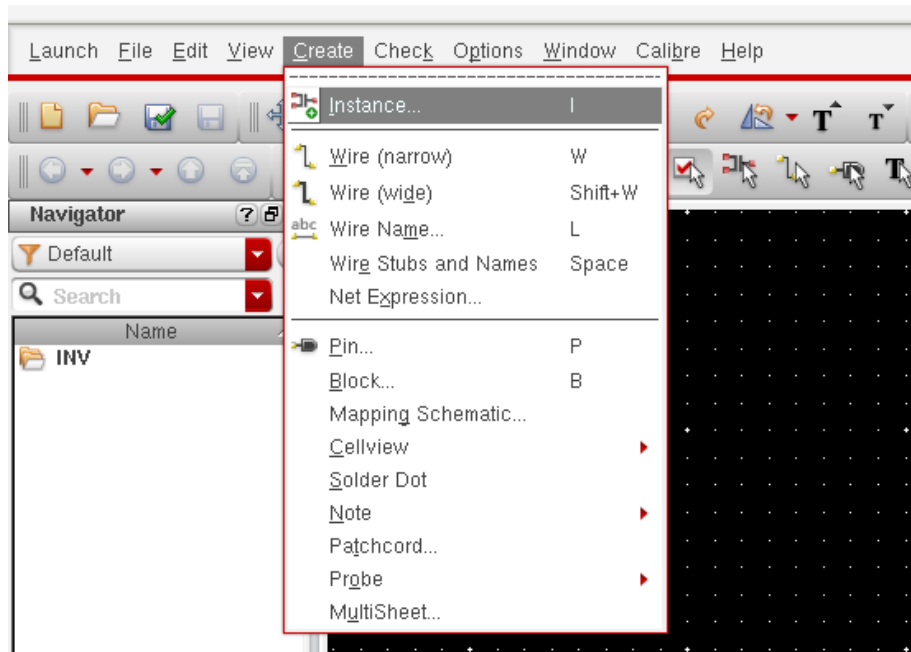
5. Place the components
 - a. In the tool bar on the top of the editor, click **Create**, and then click **Instance**



- b. Click **Browse**, the **Library Browser – Add Instance** windows will pop up



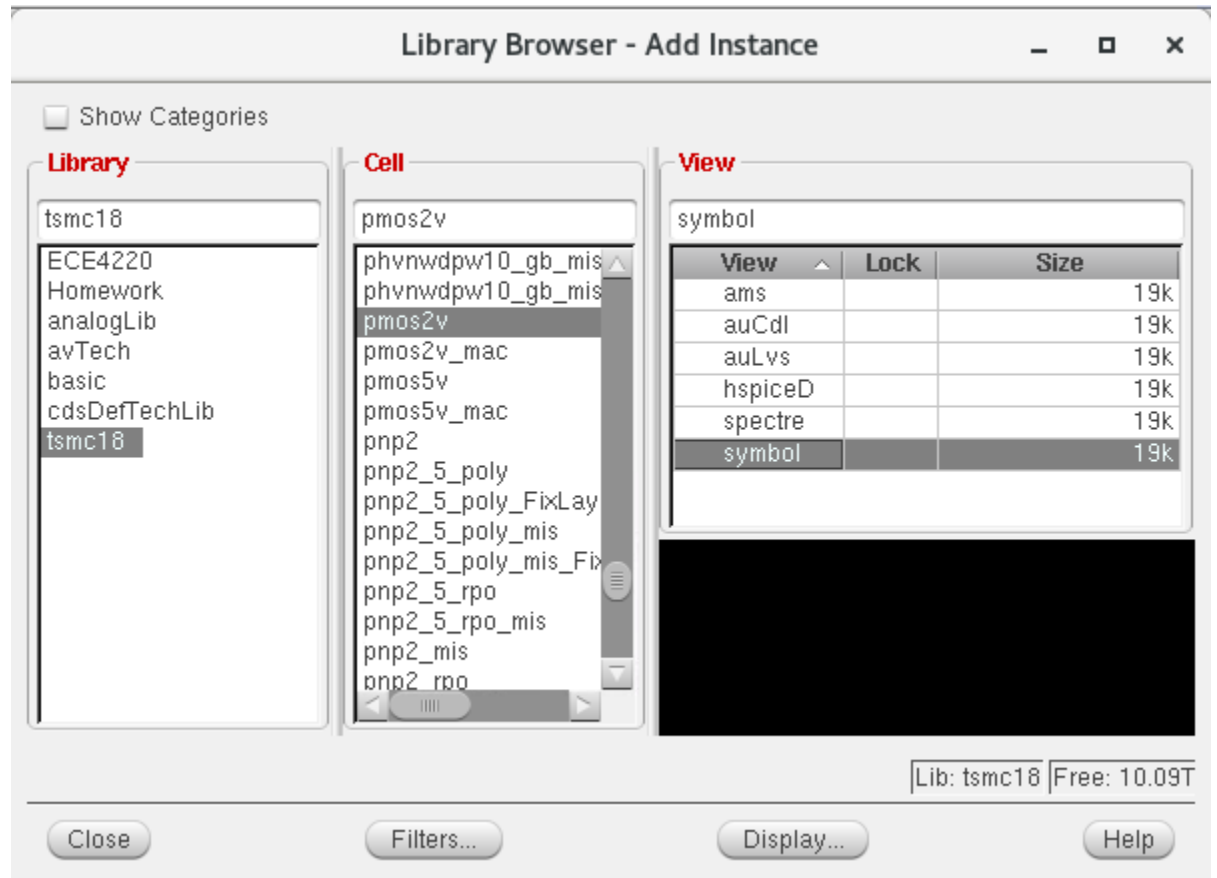- c. Click **tsmc18** under **Library**, and select **pmos2v** under **Cell**, and select **symbol** under **View**, and click **Close**



- d. Put the PMOS on the schematic
- e. Do the same for NMOS (cell name: **nmos2v**)
- f. Analog components such as voltage source, current source, ground can be found under the Library **analogLib**

- g. For input, use **“vpulse”**, right click on the component, click **Properties**, and set it up as below

Edit Object Properties

View Name: symbol off

Instance Name: V1 off

Add Delete Modify

User Property Master Value Local Value Display


Ivsignore: TRUE off

CDF Parameter	Value	Display
Frequency name for 1/period		off
Noise file name		off
Number of noise/freq pairs	0	off
DC voltage		off
AC magnitude		off
AC phase		off
XF magnitude		off
PAC magnitude		off
PAC phase		off
Voltage 1	0 v	off
Voltage 2	1.8 v	off
Period	10u s	off
Delay time		off
Rise time		off
Fall time		off
Pulse width	5u s	off
Temperature coefficient 1		off
Temperature coefficient 2		off
Nominal temperature		off
Type of rising & falling edge		off

OK Cancel Apply Defaults Previous Next Help

- i. For VDD, use **“vdc”**, do the same as for **“vpulse”**, and set **DC Voltage to 1.8 V.**

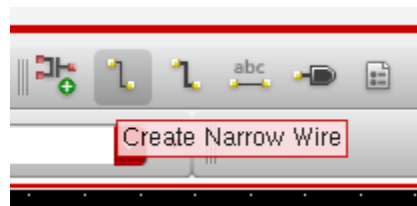
- h. To connect the components, select **Create Narrow Wire** in the tool bar



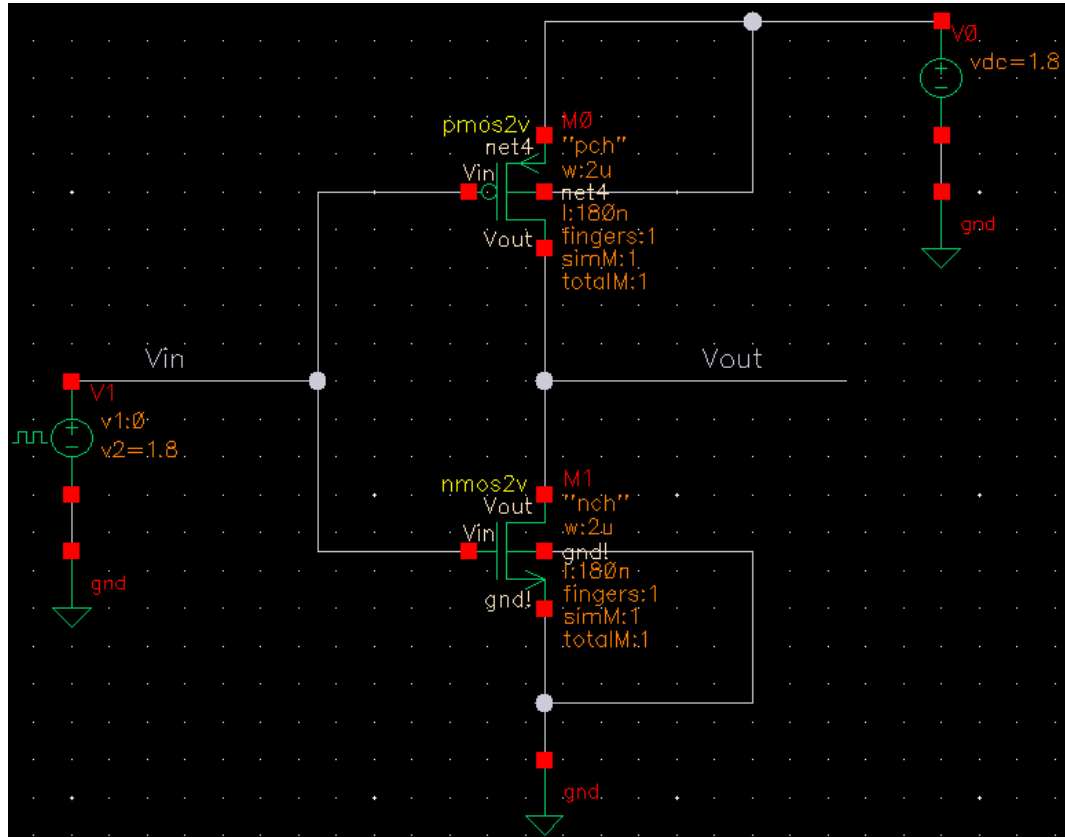- i. You may name the wires (signals) by using **Create Wire Name**, and put the tag on the wires (signals)




- j. Below is the complete schematic for an inverter




- k. Click **Check and Save** after you finish your schematic.

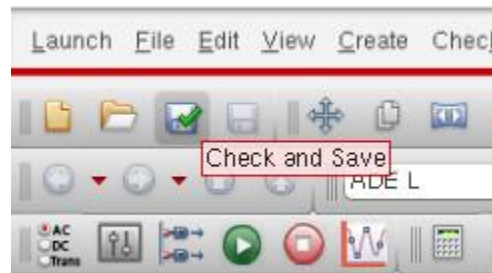
Note: Make sure you do so **every time** after you edit your schematic, otherwise errors will occur when you do simulations



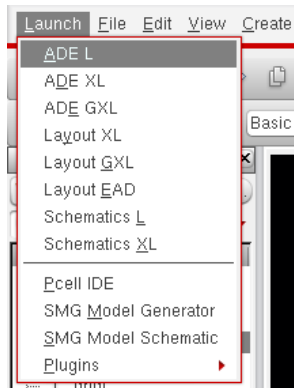
6. Run a transient simulation
 - a. Click **Launch**, and then click **ADE L**



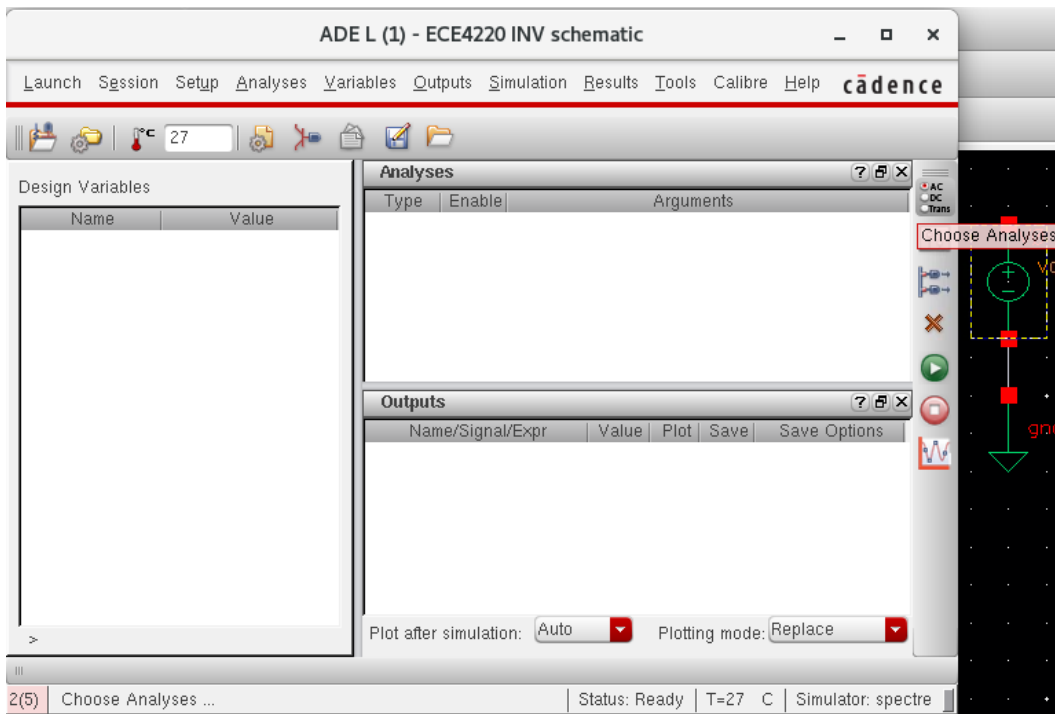
- b. In the **ADE L** window, click **Choose Analyses**



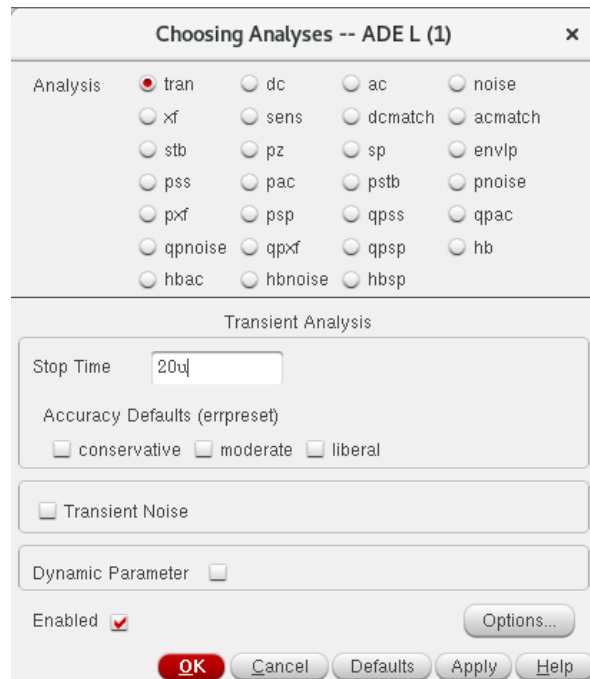- c. Set **Stop Time** to **20u**, check **Enabled**, and click **OK**



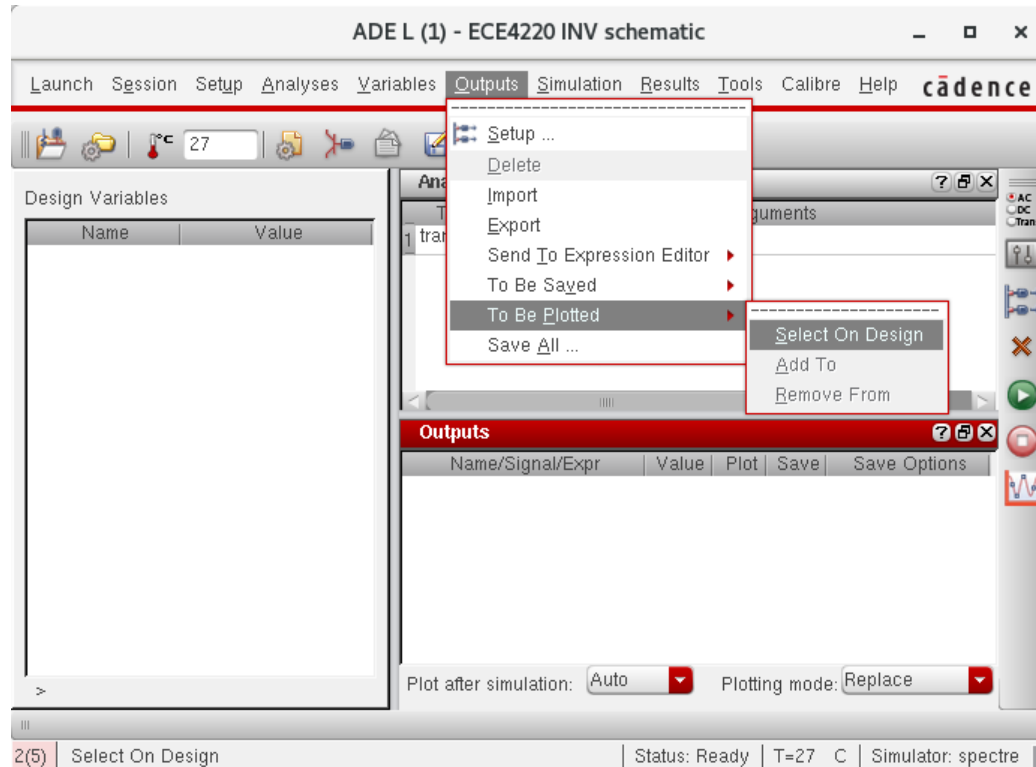- d. In the **ADE L** window, click **Outputs**, then **To Be Plotted** and then **Select On Design**



g. The plot window will pop up automatically

