
Silicon RF Phased Array at X-, Q-, W-Band and Beyond

Kwang-Jin Koh

**Virginia Tech
email: kkoh@vt.edu**

February 19, 2012


Outline

- Introduction
 - Discrete phased array: example


- Phase shifter design
 - Active phase shifter
 - Some comparisons with passive one

- Phased array designs
 - X-band receiver
 - Q-band transmitter & receiver
 - W-band & beyond

- Conclusion

 


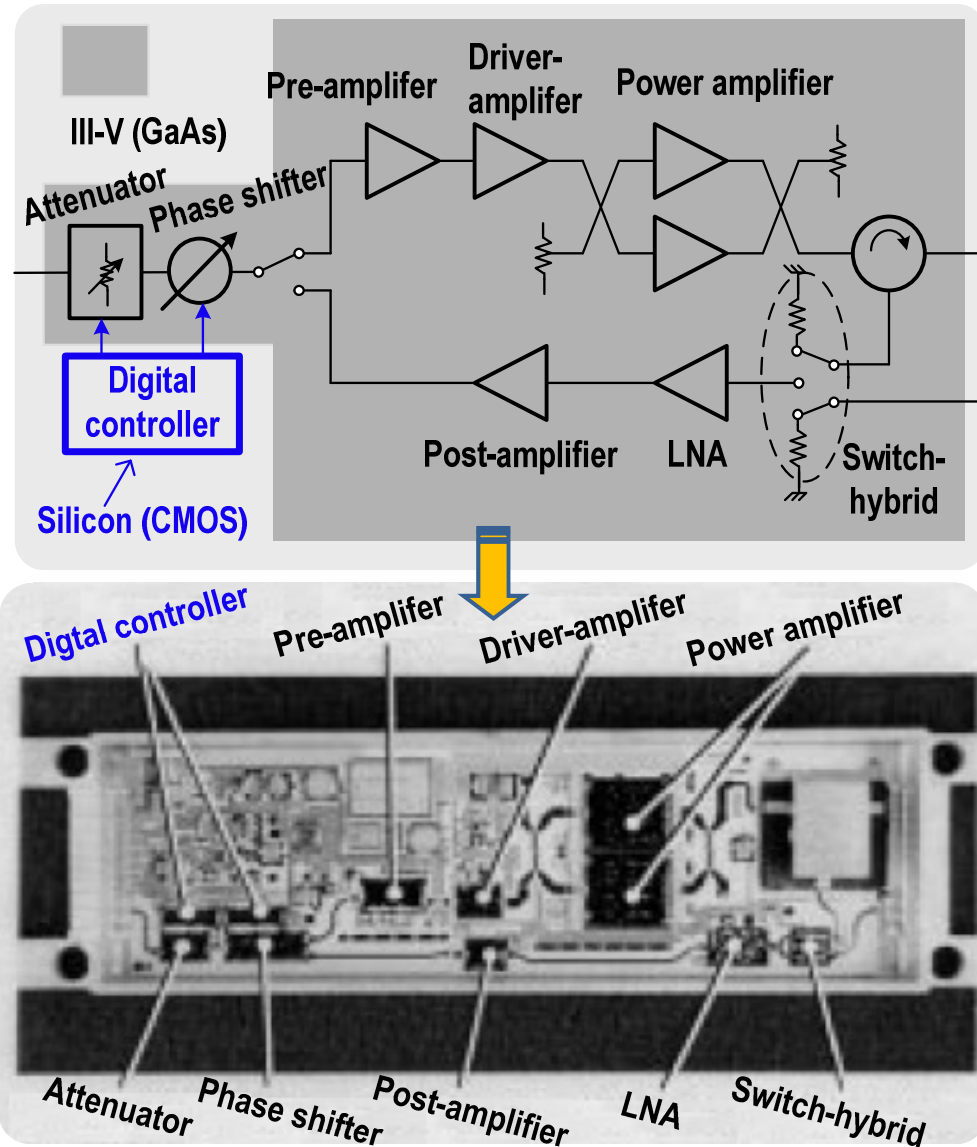Discrete design (single element, X-band: 8-12 GHz)



TYPICAL T/R MODULE IMPLEMENTATION



(B.A. Kopp, T-MTT, 2002)

 

T/R module cost elements **(\$200-2000)**
 (@ typical performance at X-band)

- III-V (GaAs) technology
- Discrete implementation: expensive & bulky
- 50- Ω interface results in high power consump.

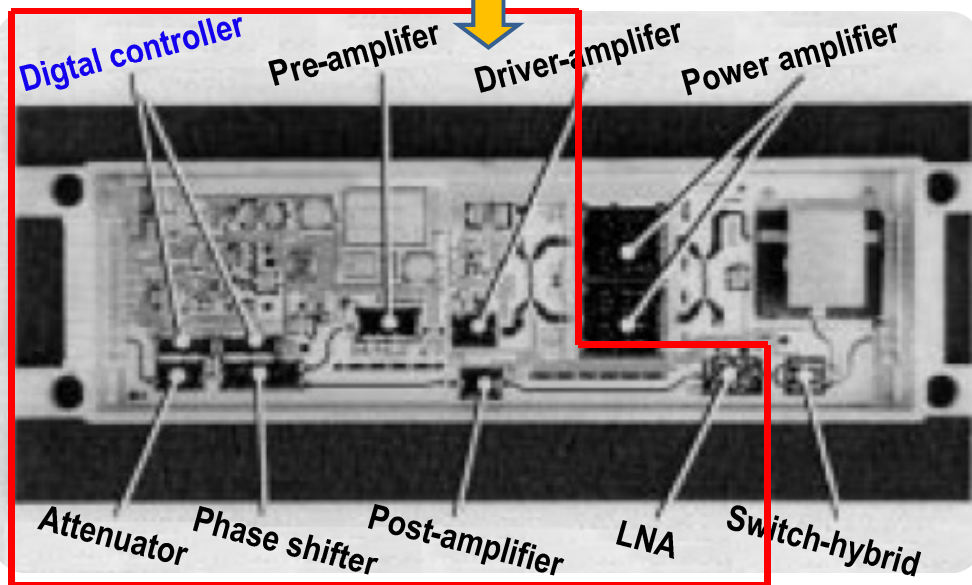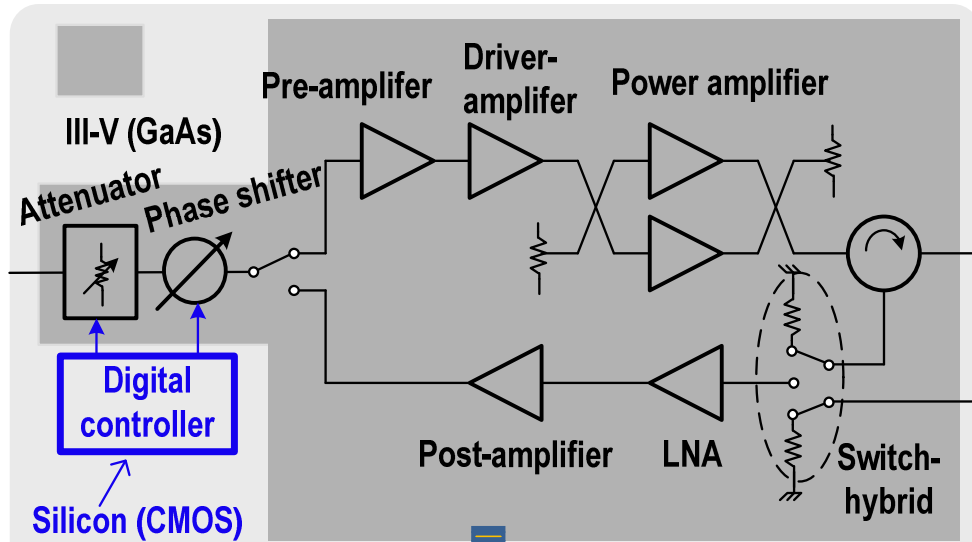
Discrete design (single element, X-band: 8-12 GHz)



INTEGRATE THESE IN SILICON (LOW-COST PHASED ARRAY < \$ 1-10)

TYPICAL T/R MODULE IMPLEMENTATION



(B.A. Kopp, T-MTT, 2002)

 

T/R module cost elements **(\$200-2000)**
 (@ typical performance at X-band)

- Leverage recent advances in silicon tech.
- Integrate many blocks in silicon
- Low power consumption

  Example: Boeing X-band array (discrete design)



64-ELEMENT X-BAND PHASED-ARRAY TRANSMITTER

(BY BOEING, 2007 Multi-function Phased-Array Symp.)

- Applications: satellite comm.
- Freq: 8.225 GHz (BW: 400 MHz)
- Data rate: 105 Mbps (QPSK)
- Radiation: LHCP
- EIRP: 22 dBW
- Scan angle: $\pm 60^\circ$
- Phase update rate: 2°/second

- **Weight: 5 kg**
- **Envelop size: 25 x 36 x 15 cm³**
- **Power consumption: 45 W**


**Watch for these numbers !
We want to minimize them.**

- **4-bit RF phase shifter**
- **Power gain (ave): 22 dB per channel**
- **OP1dB: 18 dBm per channel**
- **PAE: 22 % (@P1dB)**
- **Temp: 0-40°C**

**Could be possible in
silicon (SiGe BiCMOS
or CMOS) !**


Integrated phased-array architectures

RF-SCANNED PHASED ARRAY

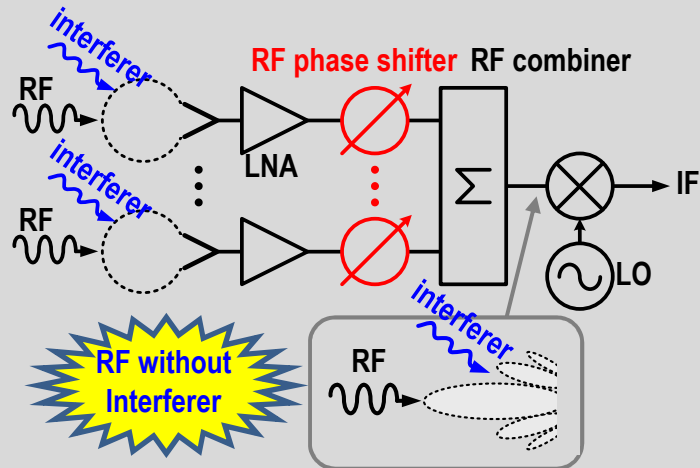

- Need 1 mixer (simple)
- Mixer “sees” high directivity pattern
- Favorable to scalability (> ~100’s # of array)
 - RF combiner can be simple, e.g. adder amp
- Widely used (since 1950)

IF (LO)-SCANNED PHASED ARRAY

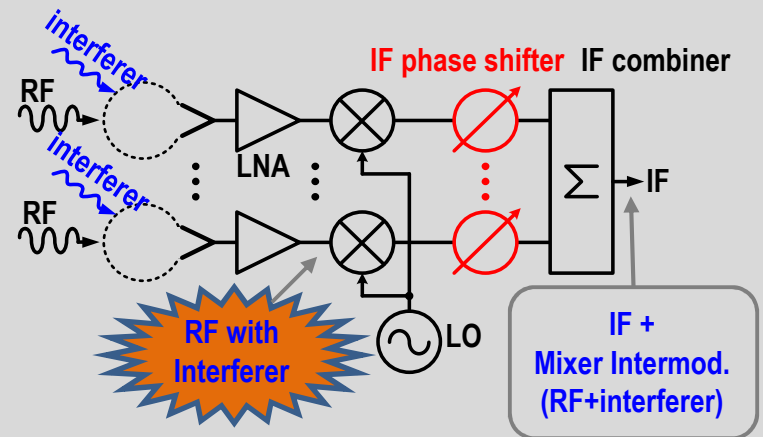


*LO-phase shifting is equivalent to IF-phase shifting

- Need # N mixers (complex)
- Mixer “sees” low directivity pattern
- Not favorable to scalability (< ~10’s # of array)
 - Complex LO distributions, coupling ...
- Limited applications


- RF-scanned array can achieve high integration level
- RF phase shifting architecture meets backward compatibility with existing systems
- **RF-scanning array is favored by industry: LM, Boeing, Teledyne, IBM, MTK, Intel, ...**

Outline

 - Introduction
 - Discrete phased array: example
- Phase shifter design
 - Active phase shifter
 - Some comparisons with passive one
- Phased array designs
 - X-band receiver
 - Q-band transmitter & receiver
 - W-band & beyond
- Conclusion




Typical passive phase shifter (example)

 


Ref: Comeau et al (Georgia Tech), "A SiGe Receiver for X-Band T/R Radar Modules", IEEE JSSC, Sept. 2008

- Freq: 8-10.7 GHz ($\Delta=2.7$ GHz, < 25% BW)
 - Phase resolution: 5-bit (11.25°)
 - RMS phase error < 9°
 - ~ 36 inductors
 - Loss ~ 20 dB
 - Area > 8 mm^2
- Issues: area & loss

LOW-PASS / HIGH-PASS APPROACH

 


Cascading many stages of this cell

 

- Blue path: low-pass
→ Phase lagging
 - Red path: high-pass
→ Phase leading
- Utilize phase difference

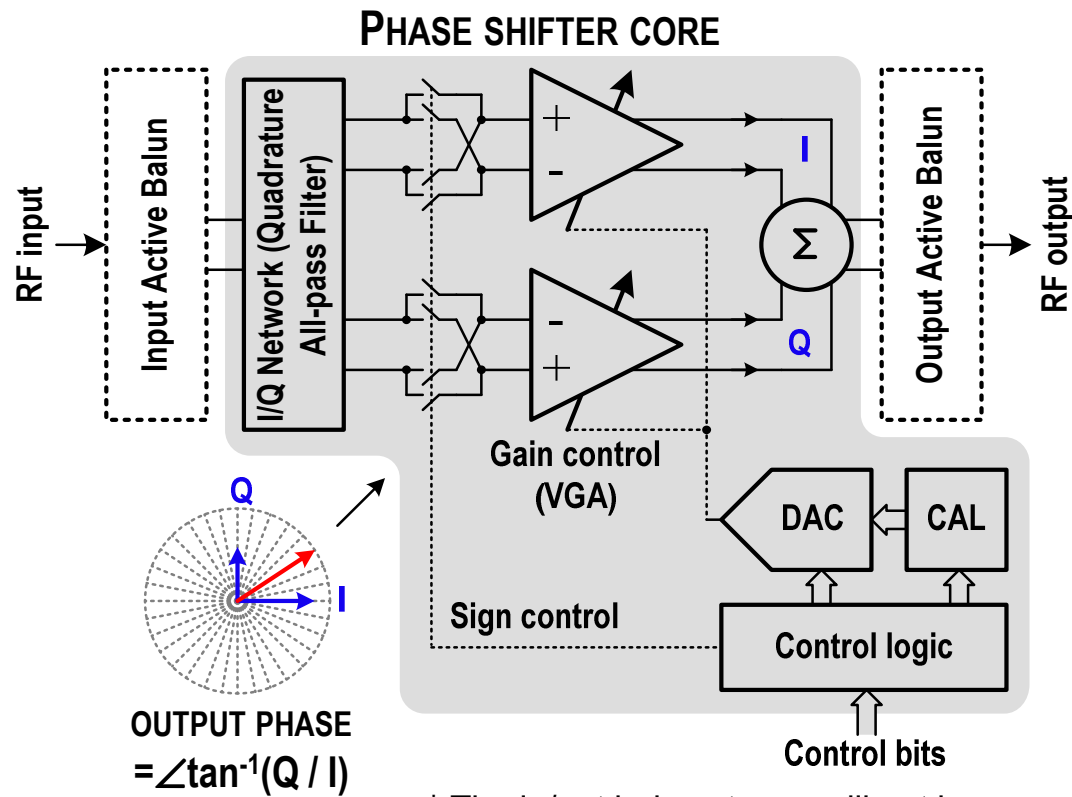Active phase shifter architecture: vector modulator




- OPERATION
- Balun provides differential signal
 - I/Q network splits signal into I & Q vector signals
 - VGA controls gain for I & Q path
 - I/Q signals are added in V-domain **(phase interpolation)**
 - DAC provides 4-bit phase control
 - CAL calibrates DAC to get 5-bit phase resolution

* The in/out balun stages will not be necessary for fully integrated differential systems

Mostly active circuits ➡ Small chip area & Gain


DAC control ➡ Fine accurate phase control & calibration

Active phase shifter - schematic

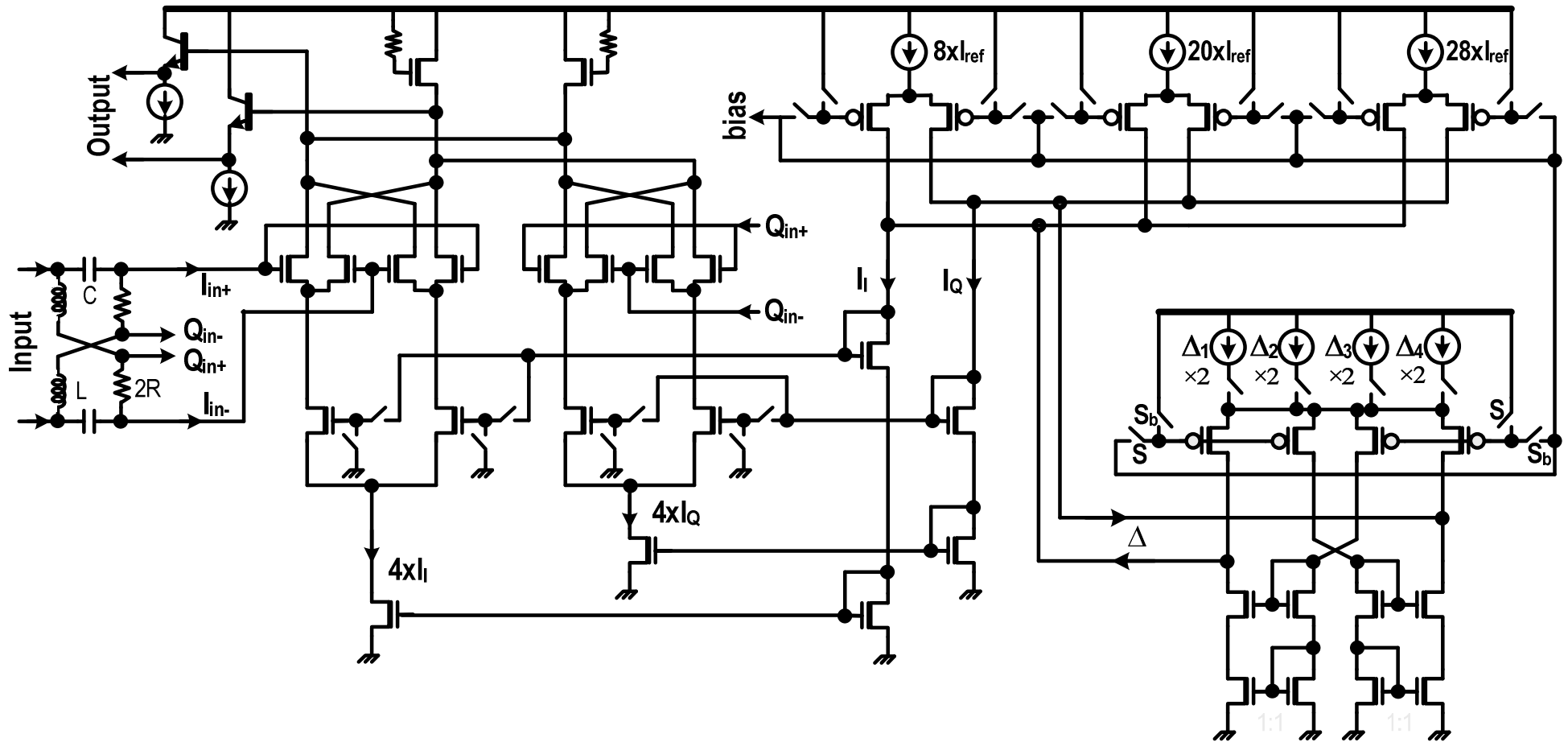


Ref: K.-J. Koh et al, "0.13- μm CMOS phase shifters for X-, Ku-, and K-Band Phased Arrays", IEEE JSSC, Nov. 2007

Active phase shifter - schematic

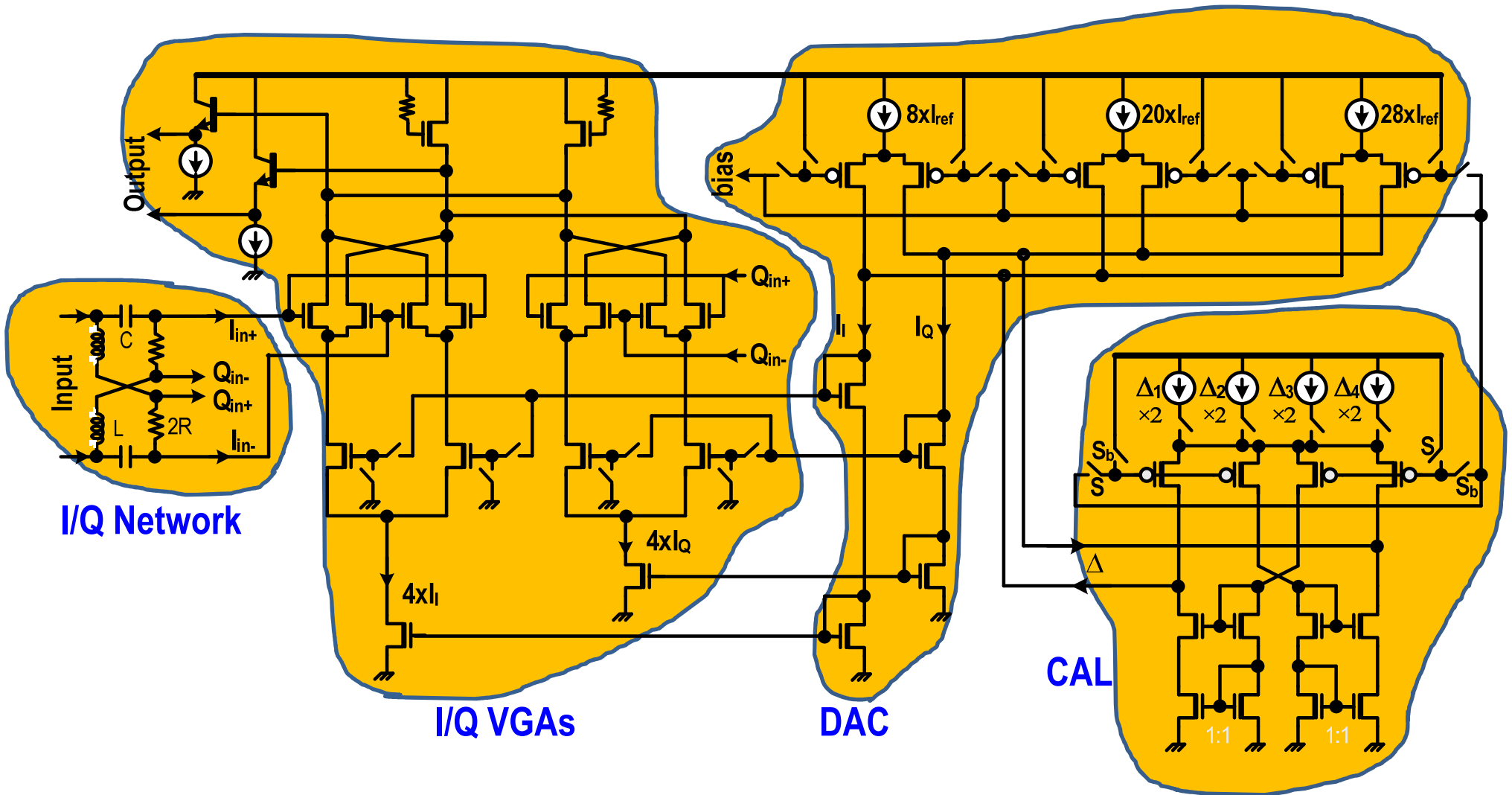

Ref: K.-J. Koh et al, "0.13- μm CMOS phase shifters for X-, Ku-, and K-Band Phased Arrays", IEEE JSSC, Nov. 2007


Active phase shifter - I/Q network

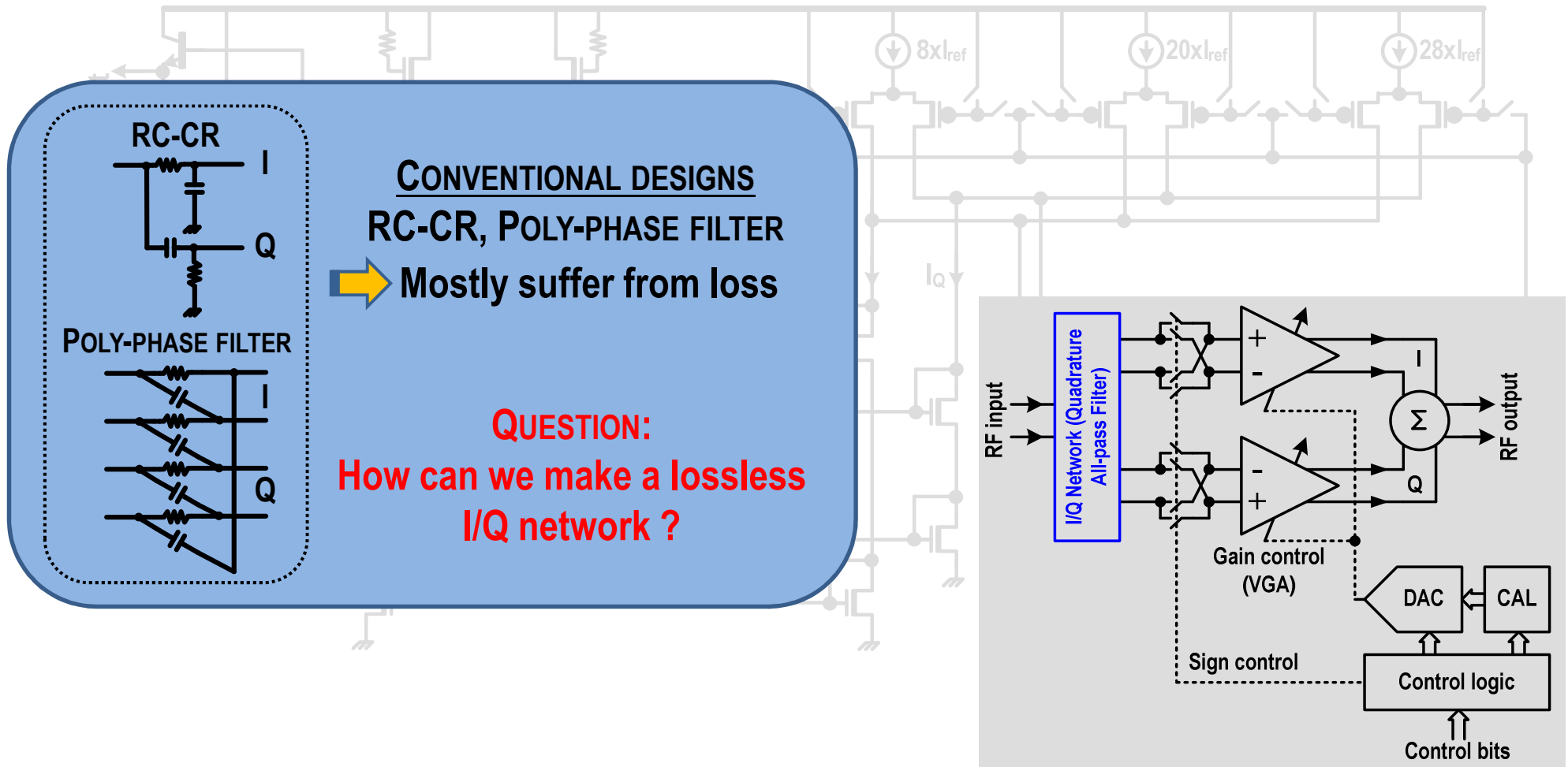



Proposed lossless I/Q network

Passive signal interpolation for quadrature vector synthesis !


1. Single-ended quadrature generation

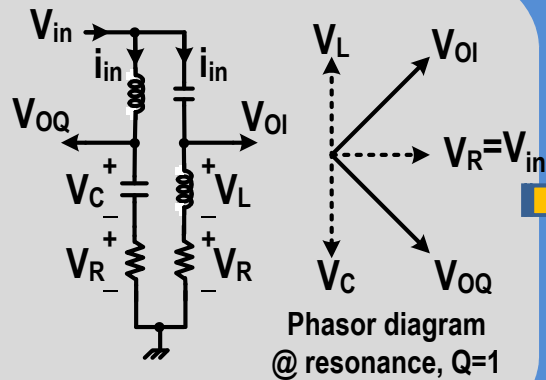

2. Differential configuration

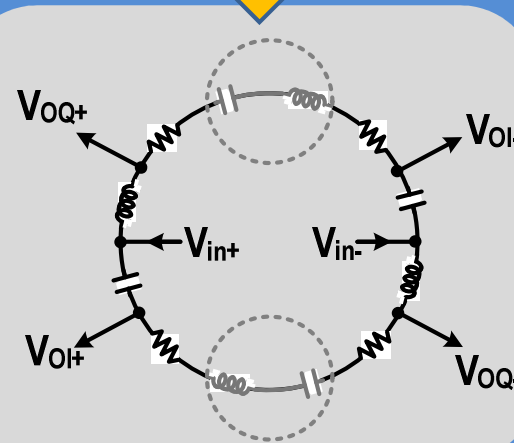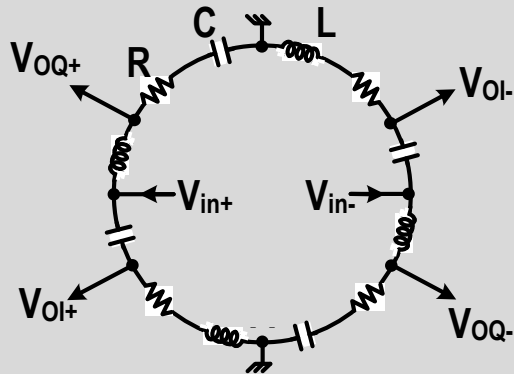

 4. Differential Quadrature All-pass Filter (QAF)



3. Elimination by series resonance

NOTE

- Step-1: 3-dB gain @ resonance
- Step-3: bandwidth extension (by removing L-C energy storage pair, de-Q)
- All-pass filter with 3dB NF




TRANSFER FUNCTION

$$\begin{pmatrix} V_{OI\pm} \\ V_{OQ\pm} \end{pmatrix} = V_{in\pm} \times \underbrace{\begin{pmatrix} s^2 + \frac{2\omega_o}{Q}s - \omega_o^2 \\ s^2 + \frac{2\omega_o}{Q}s + \omega_o^2 \end{pmatrix}}_{\substack{\text{I-path} \\ \text{Q-path}}}$$

$$\text{where, } Q = \frac{\omega_o L}{R}, \omega_o = \frac{1}{\sqrt{LC}}$$

Ref: K.-J. Koh et al, "0.13- μ m CMOS phase shifters for X-, Ku-, and K-Band Phased Arrays", IEEE JSSC, Nov. 2007

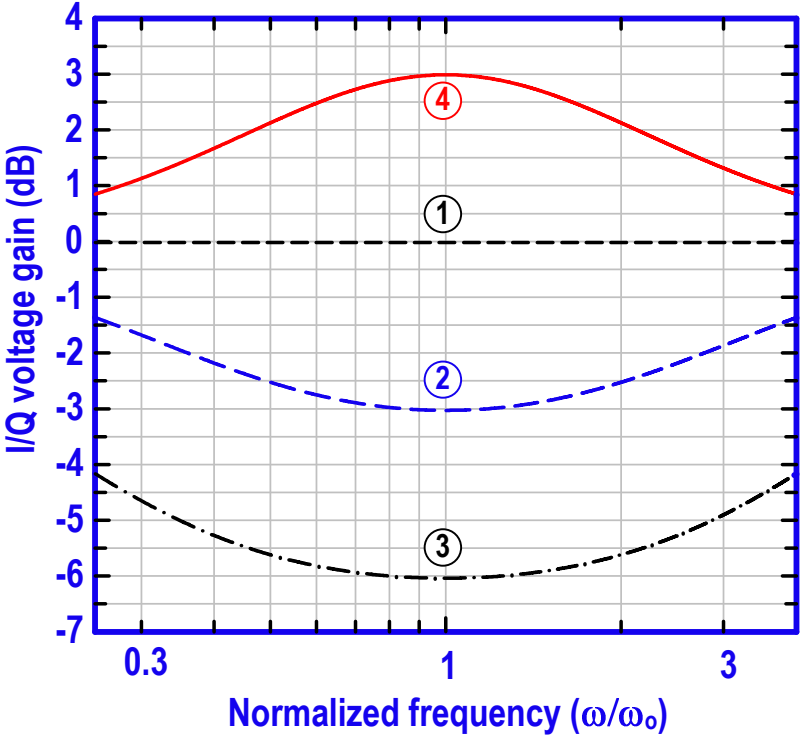  Proposed lossless I/Q network - comparison




- Exactly the same I/Q phase performance as the 2-stage polyphase filter.
- But, 6 dB larger voltage gain than the 2-stage polyphase filter.

Active phase shifter - I/Q network (lossless)



FOR X- & KU-BAND (6-18 GHz)

- $2R=50 \Omega$
 $L=324 \text{ pH}$ $\Rightarrow f_o=12 \text{ GHz}$
 $C=543 \text{ fF}$

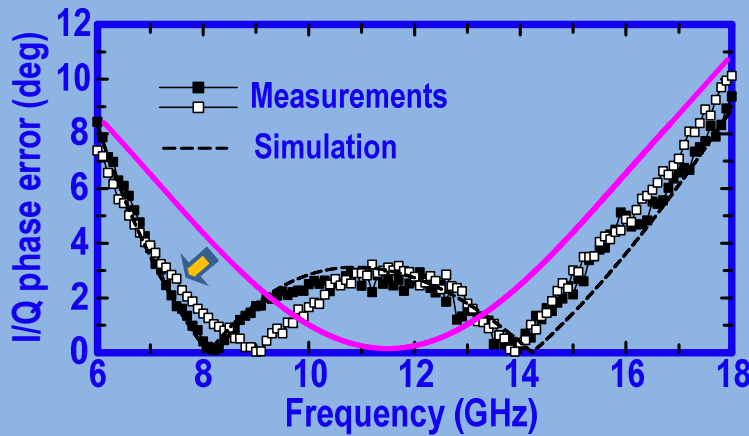
- **Optimization of R, L & C**
 \Rightarrow Allow acceptable error around f_o to increase bandwidth.



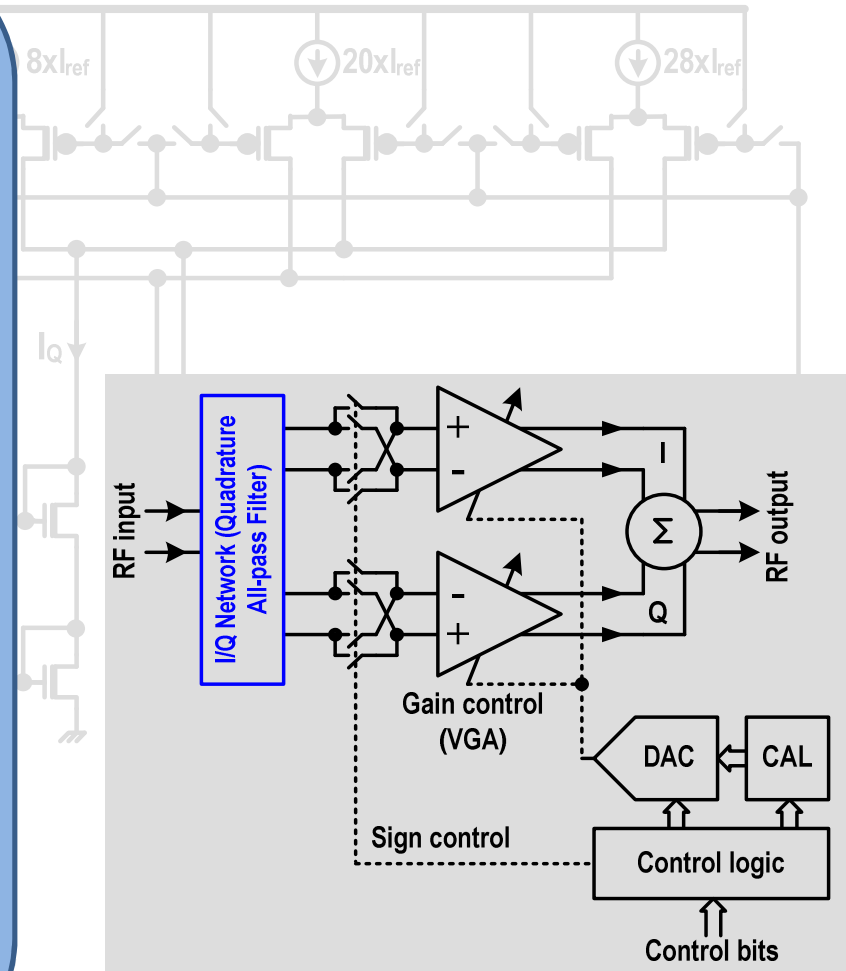 Under 70 fF loading capacitance,
I/Q phase error $< 3^\circ$ @7-15 GHz
I/Q amplitude mismatch $< 1.8 \text{ dB}$ @7-15 GHz



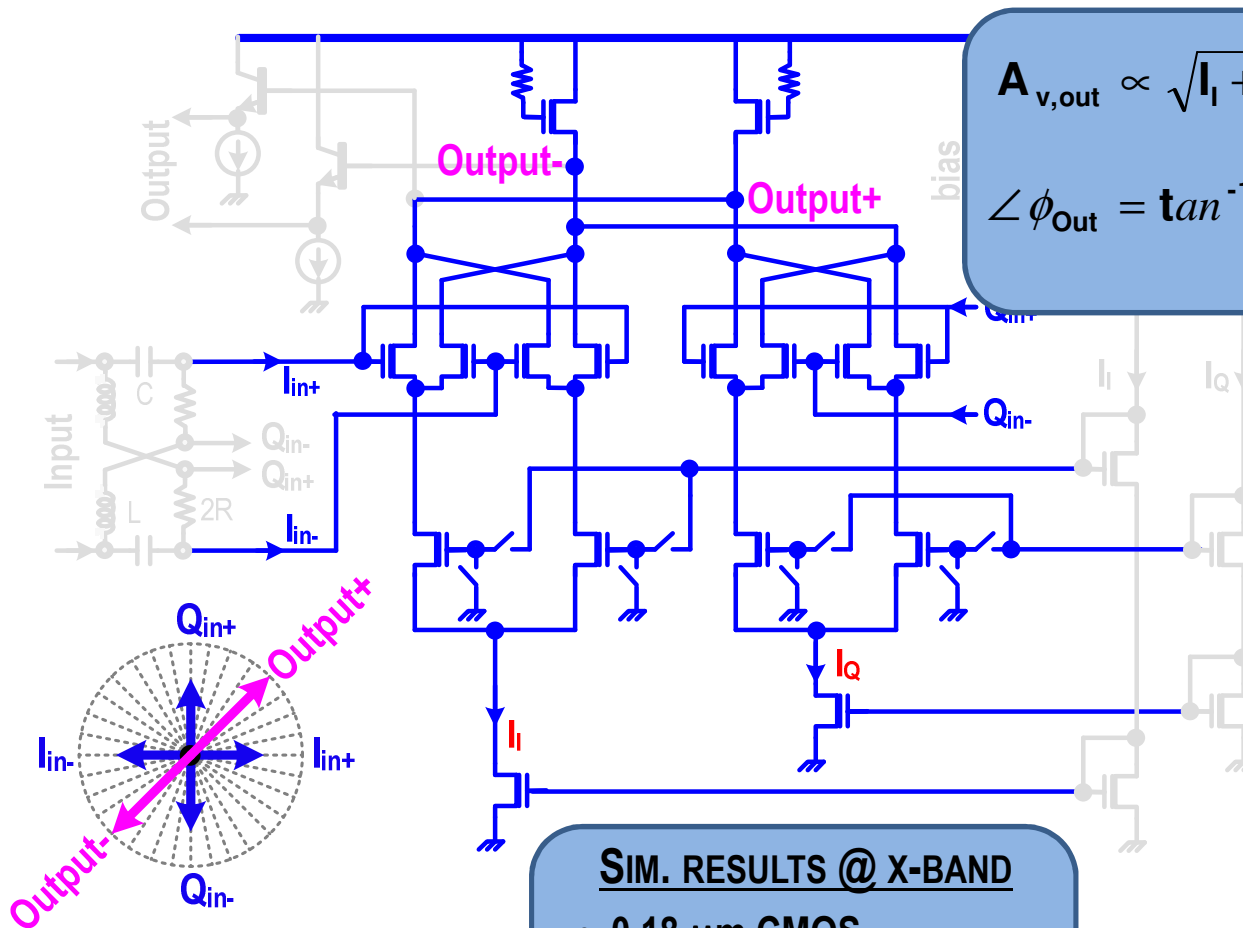Active phase shifter - I/Q VGAs (vector modulator)




$$A_{v,out} \propto \sqrt{I_i + I_q}$$

$$\angle \phi_{out} = \tan^{-1} \sqrt{\frac{I_q}{I_i}}$$

- 2 Gilbert-cells \Rightarrow I/Q VGA
- Active inductor \Rightarrow save area
- Keep $I_q + I_i = \text{constant}$ \Rightarrow constant gain versus phase change


SIM. RESULTS @ X-BAND

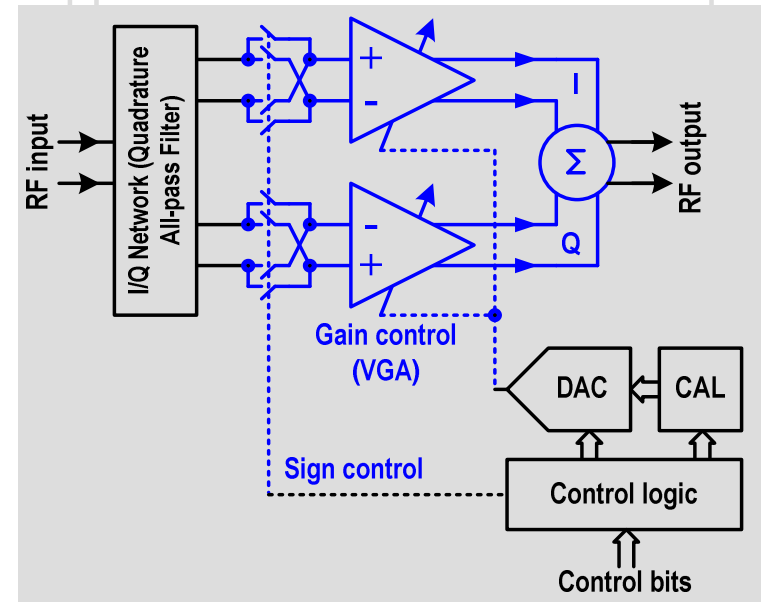- 0.18- μm CMOS
- Gain = 0 dB @12 GHz
- IIP3 = 15 dBm @12 GHz
- $I_i + I_q = 2.5 \text{ mA}$, $V_{dd} = 3.3 \text{ V}$




Active phase shifter - DAC

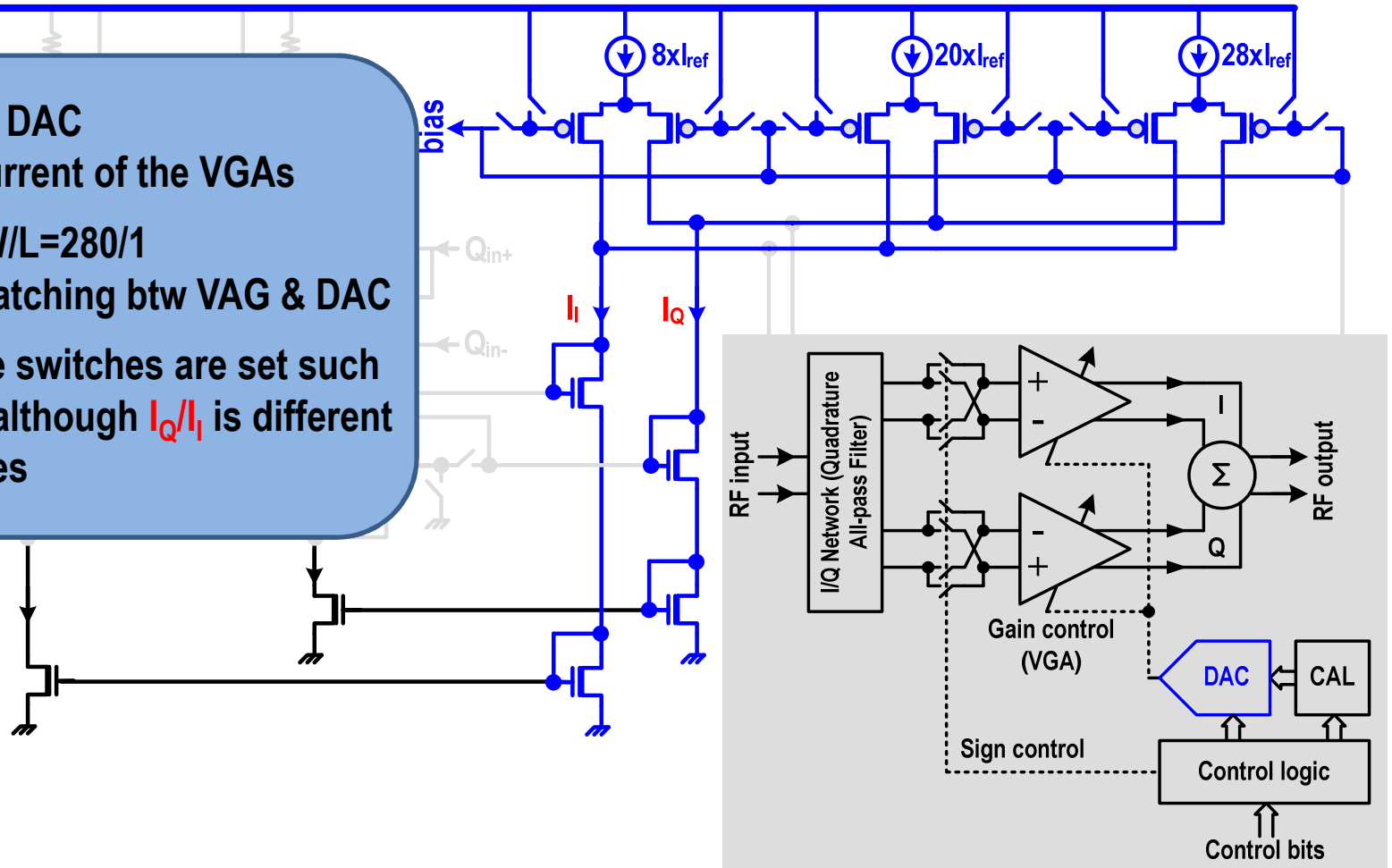- 3-bit current-scaled DAC
 → controls bias current of the VGAs
- Cascode mirror & $W/L=280/1$
 → good current matching btw VAG & DAC
- Control logic for the switches are set such that $I_I + I_Q = \text{constant}$ although I_Q/I_I is different for 4-bit phase states




Active phase shifter - CAL

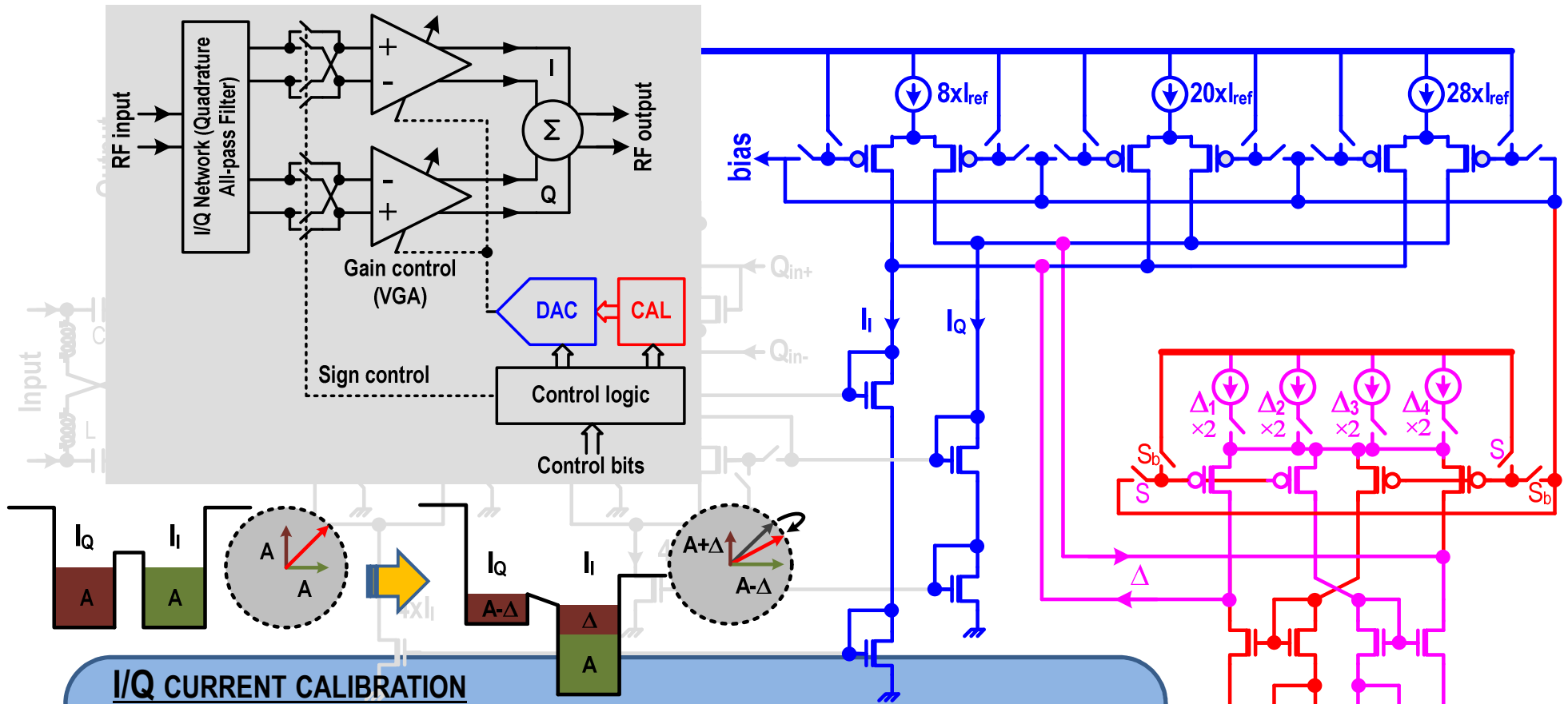


I/Q CURRENT CALIBRATION

- When **S=ON**, Δ is added to I_I and is subtracted from I_Q (by the cascode mirror).
➡ **Calibrated phase** = $\angle \tan^{-1} \left\{ \sqrt{\frac{I_Q - \Delta}{I_I + \Delta}} \right\}$
- When **S=OFF**, the direction of Δ is reversed.
- Still, $I_I + I_Q = \text{constant}$ ➡ gain is same after calibration.


Active phase shifter – chip photo

 

Active phase shifter – chip photo

 

 
- 0.18- μm SiGe BiCMOS process
(Phase shifter: 0.18- μm CMOS)
- Chip size: 1.2 x 0.7 mm²
(Phase shifter: 0.4 x 0.3 mm²)
- Total current: 18.7 mA ($V_{DD}=3.3$ V)



- Supported by “DARPA SMART project” (2006-2008)
- Presented at the DARPA meeting & MTT-s 2010
- Lockheed Martin bought the designs (schematic & layout), 2009

- All pads are ESD protected
(HBM rating: 3kV, 2A)

 Active phase shifter – 4/5-bit relative phases



After DAC calibration



(Relative phases referenced to 0°-bit phase, RMS phase error < 5.6° @6-18 GHz)

NOTE

- Phase interpolation is an independent process of frequency
- Operational BW is limited by the I/Q network, i.e. the accuracy of I/Q network
- Phase can be easily calibrated using a high resolution DAC (not easy in passive design)


First realization of integrated 5-bit active phase shifter in silicon
achieving 6-18 GHz coverage (3:1 BW)

 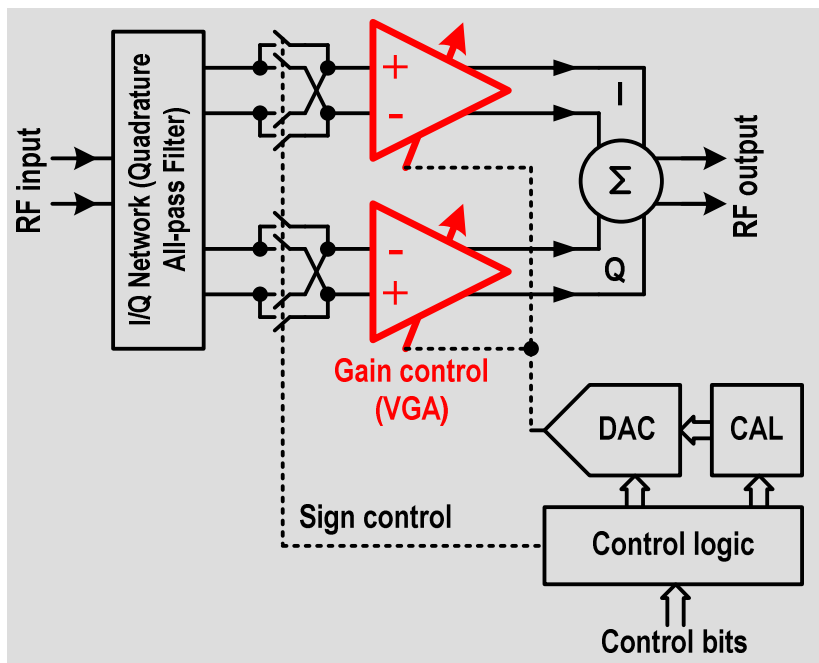Active phase shifter – temperature measurements




- I & Q paths are biased with a reference PTAT circuit
- Output phase depends on I:Q gain ratio (not absolute gain)
- I & Q amplifiers track each other vs. PVT, resulting in low sensitivity to PVT
- RMS phase error $< 6^\circ$ @ 25°-100° C

 Comparison: **passive** vs. **active** phase shifter



Ref: Comeau et al (Georgia Tech), "A SiGe Receiver for X-Band T/R Radar Modules", IEEE JSSC, Sept. 2008

 - Freq: 8-10.7 GHz ($\Delta=2.7$ GHz, **< 25% BW**)
- Phase resolution: 5-bit (11.25°)
- **RMS phase error < 9°**
- **~ 36 inductors**
- **Loss ~ 20 dB**
- **Area > 8 mm² (> 65x active design)**



Ref: K.-J. Koh et al, "0.13- μ m CMOS phase shifters for X-, Ku-, and K-Band Phased Arrays", IEEE JSSC, Nov. 2007


Ref: K.-J. Koh et al, "A 6-18 GHz 5-bit active phase shifter", IEEE MTT-S, May 2010

- Freq: 6-18 GHz ($\Delta=12$ GHz, **3:1 BW**)
- Phase resolution: 5-bit (11.25°)
- **RMS phase error: < 5.6°**
- **2 inductors**
- **Loss ~ 0 dB**
- **Area: 0.12 mm² (smallest one published)**


Compare

Outline

 
- Introduction
 - Discrete phased array: example
- Phase shifter design
 - Active phase shifter
 - Some comparisons with passive one
- Phased-array designs
 - X-band receiver
 - Q-band transmitter & receiver
 - W-band & beyond
- Conclusion



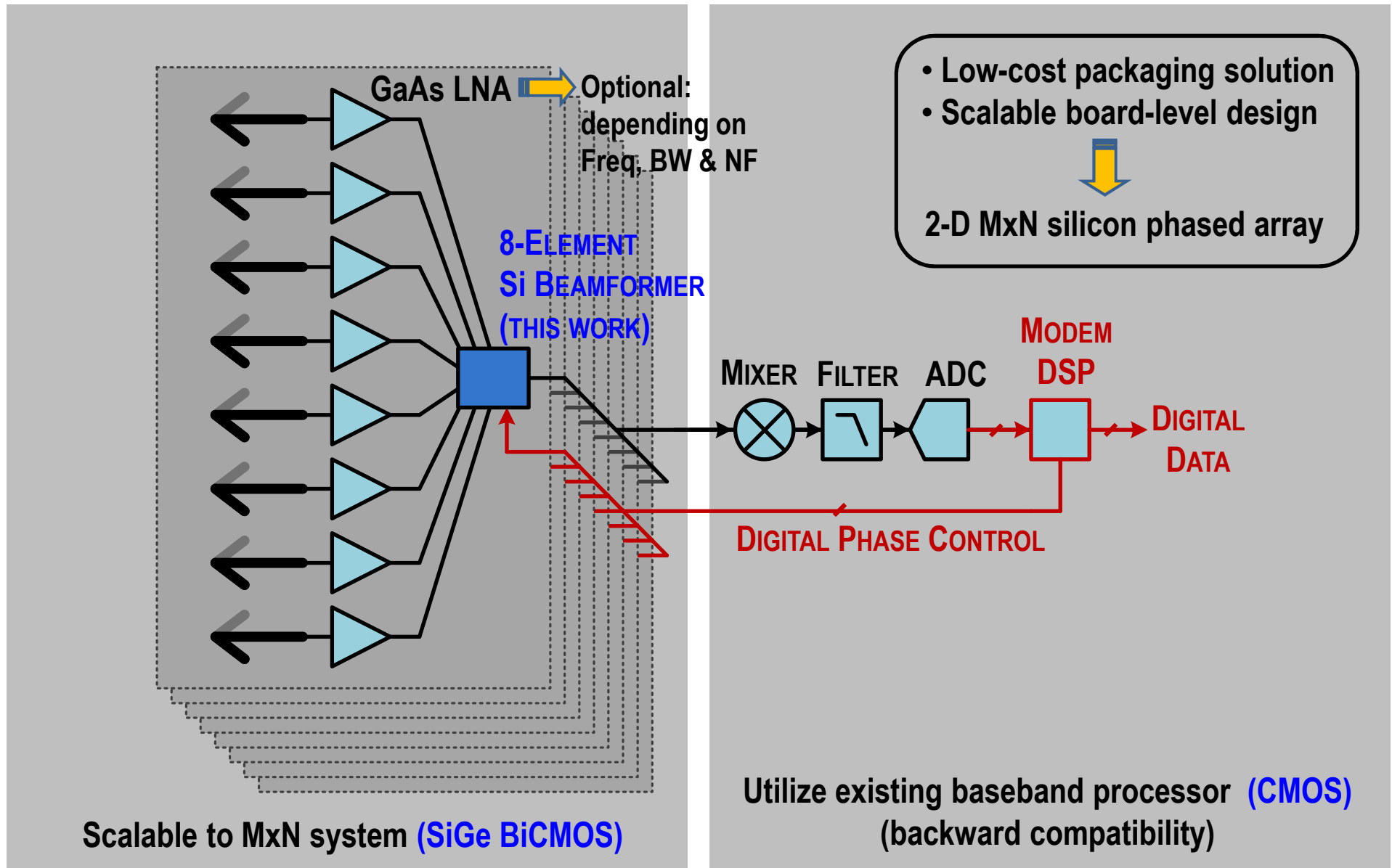8-element phased-array (6-18 GHz, **scalable array**)




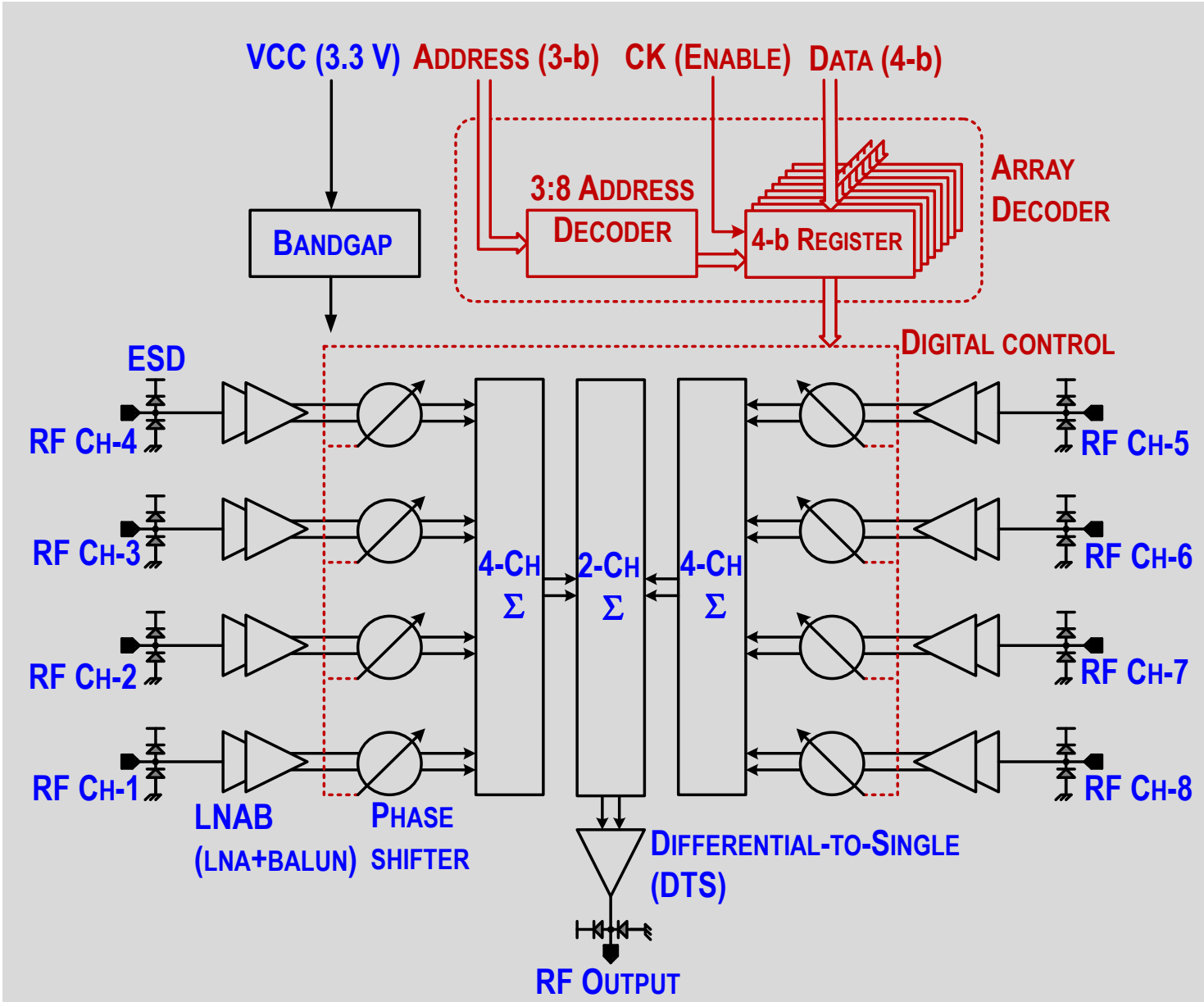8-element phased-array (6-18 GHz, architecture)




- Integrate 8-CHs in SiGe
- Integrate “RF + DIGITAL”
- 4-bit active phase shifter
- 2-step signal combining (active adders)
- ESD protection (3kV, 2A)

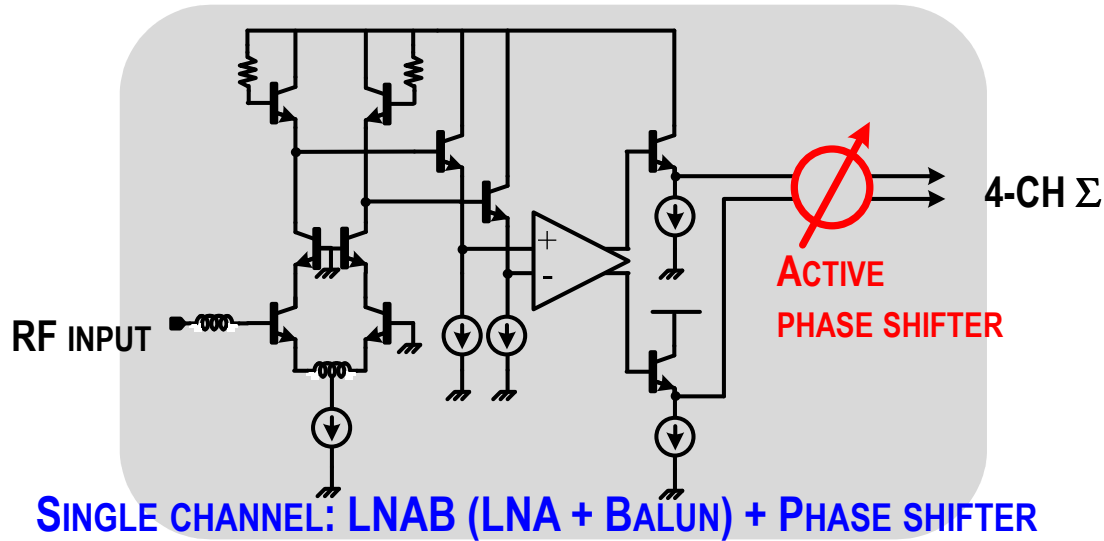8-element phased-array (6-18 GHz, schematics)




- Emitter-coupled diff-pair
- Single-to-differential conversion
- L-C input matching
- 2nd-stage diff amp: CMRR

 
- Signal $-\Sigma$ in current domain
- Binary fashion signal $-\Sigma$
- Wideband signal- Σ
- NMOS-based push-pull



 
8-element phased-array (6-18 GHz, chip photo)






 
8-element phased-array (6-18 GHz, chip photo)






 
- 0.18- μm SiGe BiCMOS (Jazz SiGe120, 1P6M, $f_T=150$ GHz)
- Area = 2.2 x 2.4 mm²
- Near perfect corporate-feed layout (E-length btw any input to output is identical)
- Metallic barrier: max CH-CH isolation
- $V_{CC}=3.3$ V, $I_{total}=170$ mA (561 mW, Active- $\Sigma < 10\%$)



   
 
8-element phased-array (6-18 GHz, gain, NF, matching)



 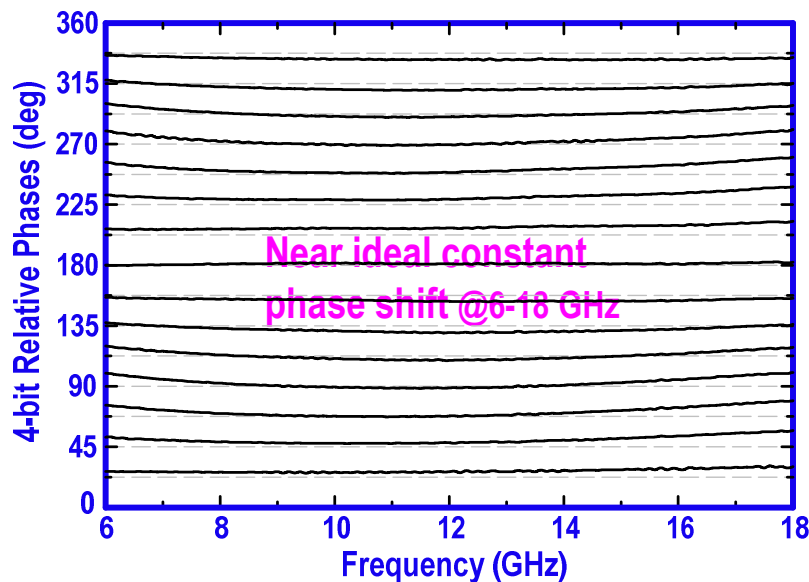  8-element phased-array (6-18 GHz, phase, group delay)




  8-element phased-array (6-18 GHz, ch-to-ch variation)




- Comparison of 128 S-Parameters
= 8 (channels) x 16 (4-bit phases)
- Excellent matching between array elements
→ Major benefit in the on-chip integration

 8-element phased-array (6-18 GHz, ch-to-ch coupling)




 SIGNAL ERROR DUE TO COUPLING
(@ 12 GHz, GAIN=20 dB)



- Coupling causes amplitude & phase errors which could be serious in silicon
- Measured errors are negligible due to high isolation layout, e.g. metallic barrier

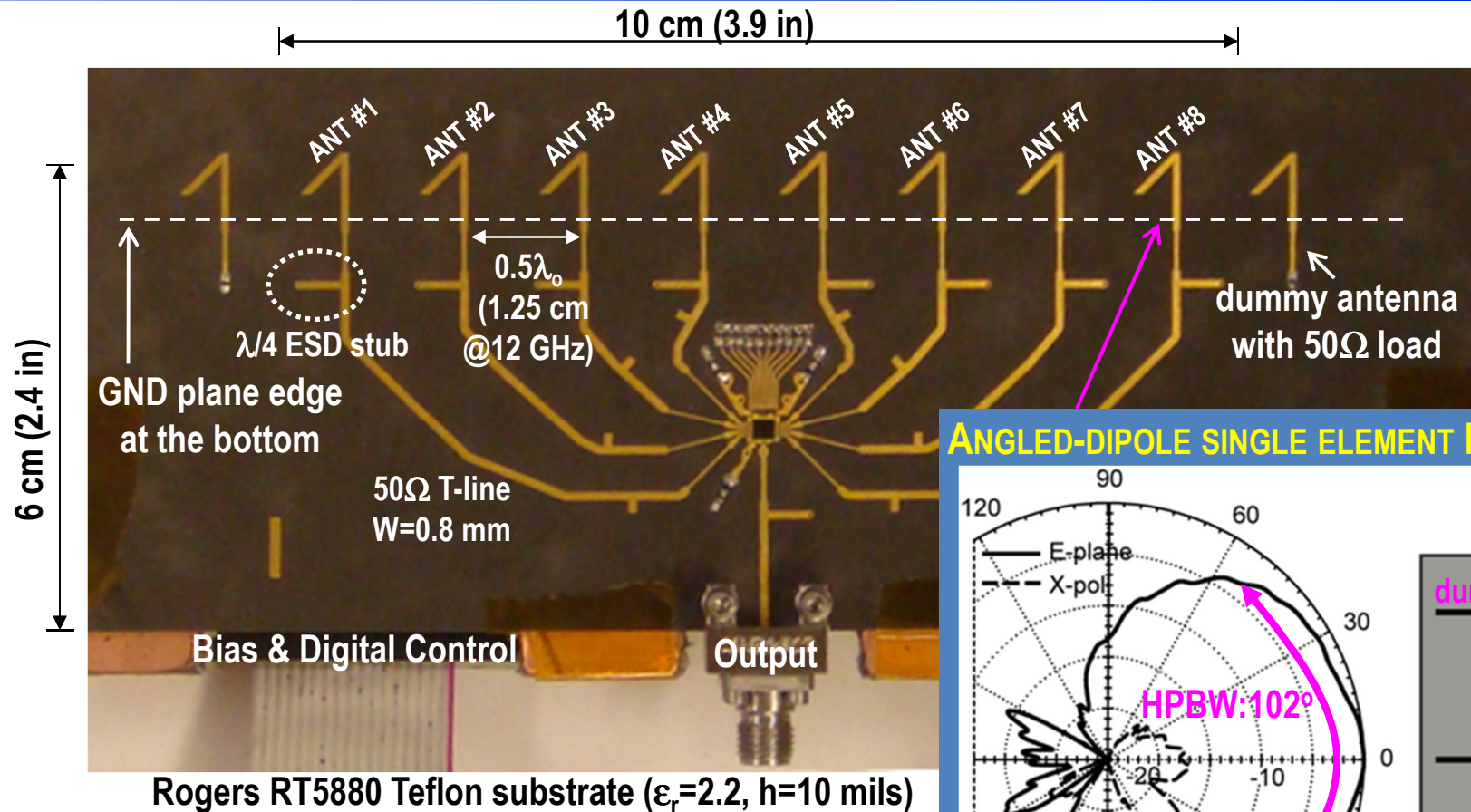8-element phased-array (6-18 GHz, chip-on-board, angled-dipole)




ANGLED-DIPOLE ANTENNA:

Wider beam width, Lower mutual coupling, Wideband S11

HPBW: 102°, S11 < -10 dB @10.5-14 GHz, S21 < -17 dB


Scan angle: +/- 60° w/ 4dB drop in element factor

ANGLED-DIPOLE SINGLE ELEMENT E-PATTERN


 


Ref: Y. A. Atesal, B. Cetinoneri, [K.-J. Koh](#), G. M. Rebeiz, "X/Ku-Band 8-Element Phased Arrays Based on Single Silicon Chips", 2010 IMS, May 2010

 8-element phased-array (6-18 GHz, chip-on-board, chip mounting)




BONDWIRE & COUPLING SIMULATION WITH HFSS

  




Worst-case coupling < -17 dB, bondwire inductance: 0.5 nH

 SILICON PHASED ARRAY CHIP (2.2 x 2.4 mm²)



Ref: Y. A. Atesal, B. Cetinoneri, [K.-J. Koh](#), G. M. Rebeiz, "X/Ku-Band 8-Element Phased Arrays Based on Single Silicon Chips", 2010 IMS, May 2010

  
 
8-element phased-array (6-18 GHz, chip-on-board, z-matching)



$S_{11} < -10 \text{ dB @ } 10\text{-}14 \text{ GHz}$ $S_{22} < -10 \text{ dB @ } 8.5\text{-}13.5 \text{ GHz}$

8-element phased-array (6-18 GHz, board measurement setup)

ANECHOIC ANTENNA CHAMBER

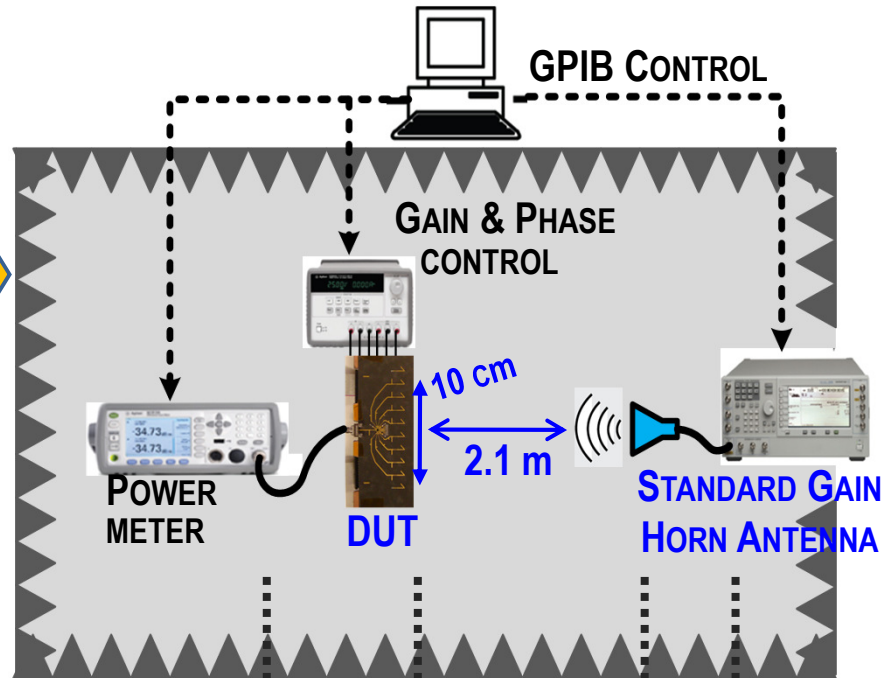 


Friis TRANSMISSION EQUATION

$$\frac{P_R}{P_T} = \underbrace{G_T}_{\text{HornANTgain} = 20 \text{ dB}} \times \underbrace{\left(\frac{\lambda}{4\pi \cdot R}\right)^2}_{\text{Freespacepathloss} = -60.5 \text{ dB}} \times \underbrace{G_R}_{\text{Phasedarraygain} = 41 \text{ dB}}$$


Channel gain (20 dB)
 Array factor (18 dB)
 Antenna gain (3 dB)

R: 2.1 m
 λ: 2.5 cm
 @12 GHz

 


8-element phased-array Rx (6-18 GHz, board measurement)

MEASURED PATTERN @12 GHz

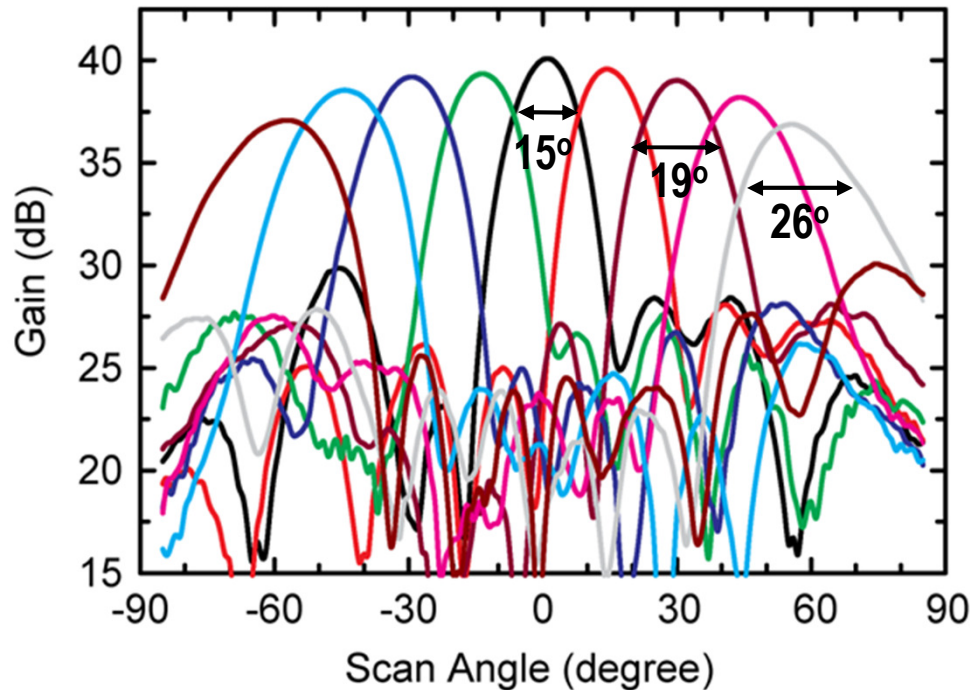

MEASURED PATTERN @11.4-12.6 GHz

 


- Scanned from -60° to 60°
- Element factor causes 3-4 dB drop at 60°
- HPBW: 15° @ 0° -scan, 19° @ 30° -scan, 26° @ 60° -scan
- Excellent agreement with simulations


- No-true-time delay on each element
- Slight beam walk @ 60° - scan angle
- Instantaneous BW limited to 11.4-12.6 GHz ($\Delta=1.2$ GHz, 10%)

First system-level (w/ antenna) demo of an X-band array based on a single silicon chip !

Area comparison: single vs. 8-array

 

 Ref: Comeau et al (Georgia Tech), "A SiGe Receiver for X-Band T/R Radar Modules", IEEE JSSC, Sept. 2008



Ref: K.-J. Koh et al, "An X- and Ku-Band 8-Element Phased-Array Receiver in 0.18- μ m SiGe BiCMOS Technology", IEEE JSSC, June 2008

Integration ($A=13.3 \text{ mm}^2$):
LNA + Phase shifter + bias c.k.t.
(single element: analog)


Just 40% area!

Compare

Integration ($A=5.3 \text{ mm}^2$):
8 LNAs + 8 Phase shifters + bandgap
(8 elements: analog)
+
Array decoder (digital control)


Outline

 - Introduction
 - Discrete phased array: example
- Phase shifter design
 - Active phase shifter
 - Some comparisons with passive one
- Phased array designs
 - X-band receiver
 - **Q-band transmitter & receiver**
 - W-band & beyond
- Conclusion



16-element Q-band phased-array Tx (large array, 3-D integration)

 
PROJECT: DARPA SCALABLE MILLIMETER-WAVE ARRAY TECHNOLOGY (SMART, 2006-2008)



- Q-band satellite comm.
(43-45 GHz, $\lambda/2=3.4$ mm)
 - Large array: 20x20 elements
 - Microstrip antenna size
= 3.4×3.4 mm²
 - Integrate 1 sub-array (4x4)
in a **single package**
(Area < 3x3 cm²)
- ↓
- Multi-layered integration**
in a **single package**

TILE-BASED 2-D LARGE ARRAY (20X20) CONSTRUCTION
ONE TILE (SUB-ARRAY): 4X4 ELEMENT, ONE SUPER-TILE: 5X5 TILES

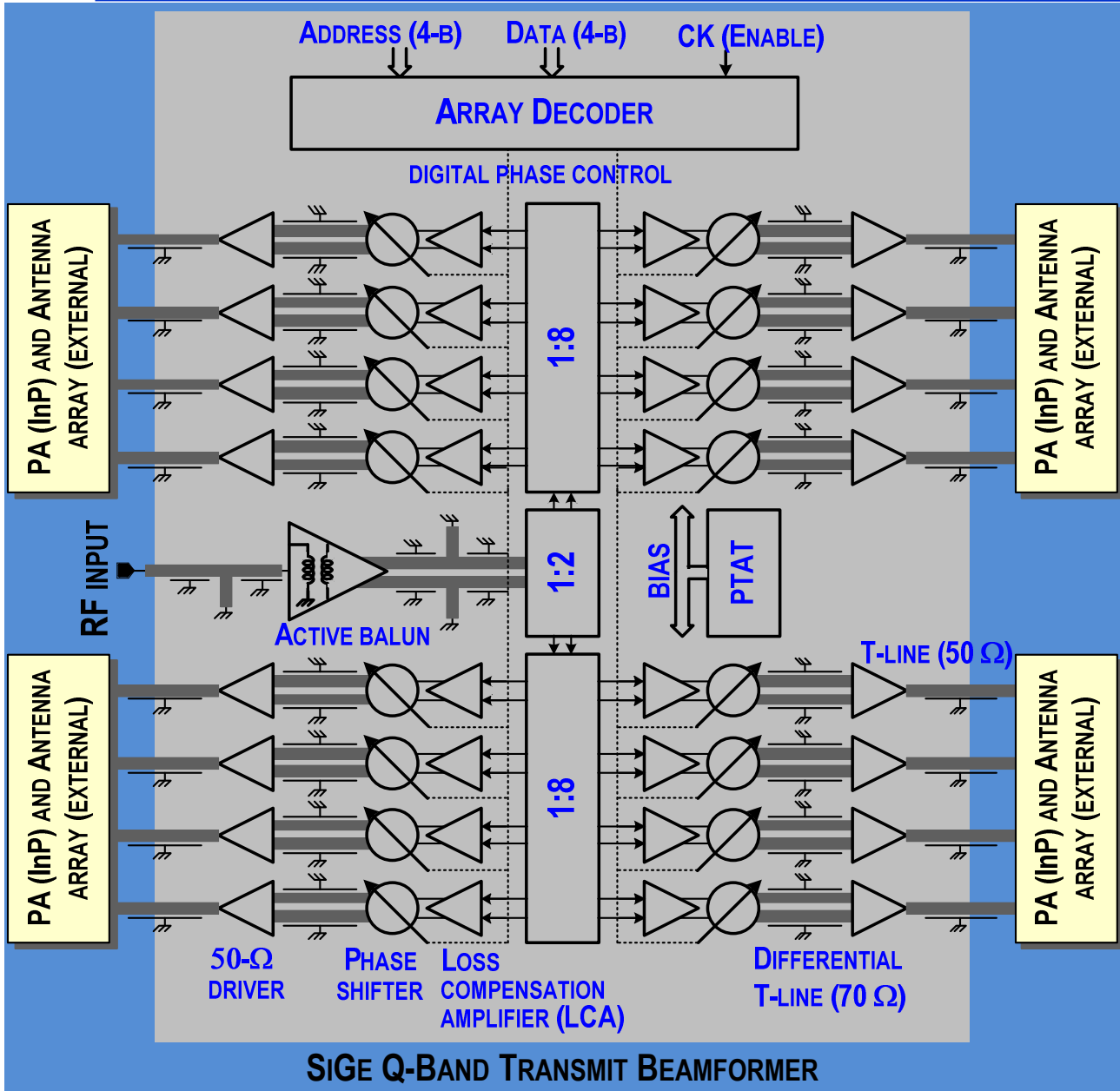
16-element Q-band phased-array Tx (44 GHz, architecture)




- 44 GHz satellite comm. application
- Integrate 16 elements (4x4)
- Corporate feed architecture
 - Active balun, 1:2 active, 1:8 passive
- Single channel elements
 - LCA: compensate 1:8 division loss
 - 4-bit active phase shifter
 - 50-Ω driver drives external PA
- Array decoder
 - control each channel independently

Ref: K.-J. Koh *et al*, "A Millimeter-wave (40-45 GHz) 16-Element Phased-Array Transmitter in 0.18-μm SiGe BiCMOS Technology", IEEE JSSC, May 2009


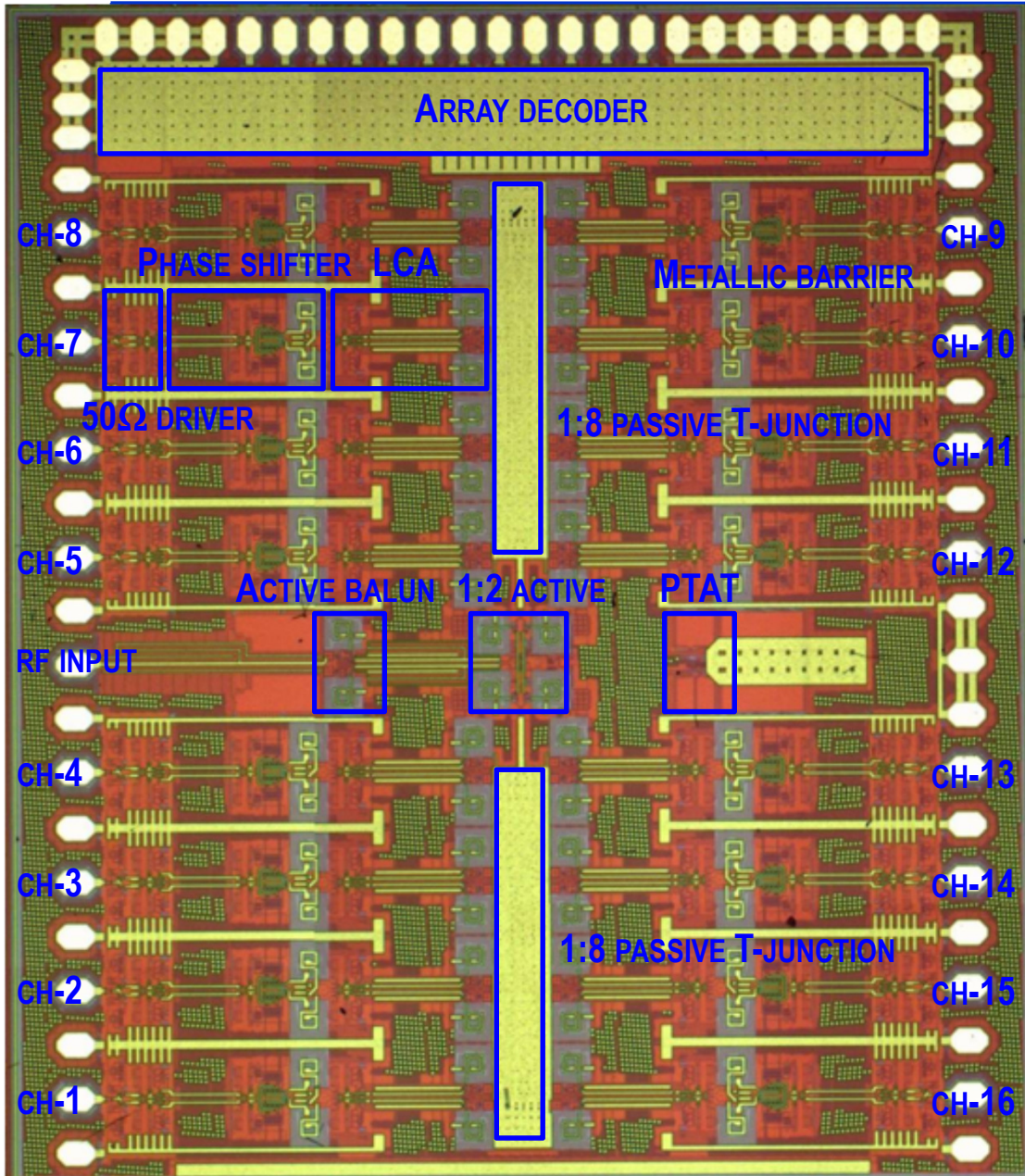
16-element Q-band phased-array Tx (44 GHz, chip photo)



 
- 0.18- μm SiGe BiCMOS technology
 - 1P6M, $f_T=150$ GHz
- Size: 2.6 x 3.2 mm² (overall)
- Near perfect corporate-feed layout
 - E-length is identical for all channels
- Metallic barrier
 - Grounded via stacks from M1-M6
 - Decrease ch-to-ch coupling
- Current consumption: 724 mA (5 V, 3.6 W)



 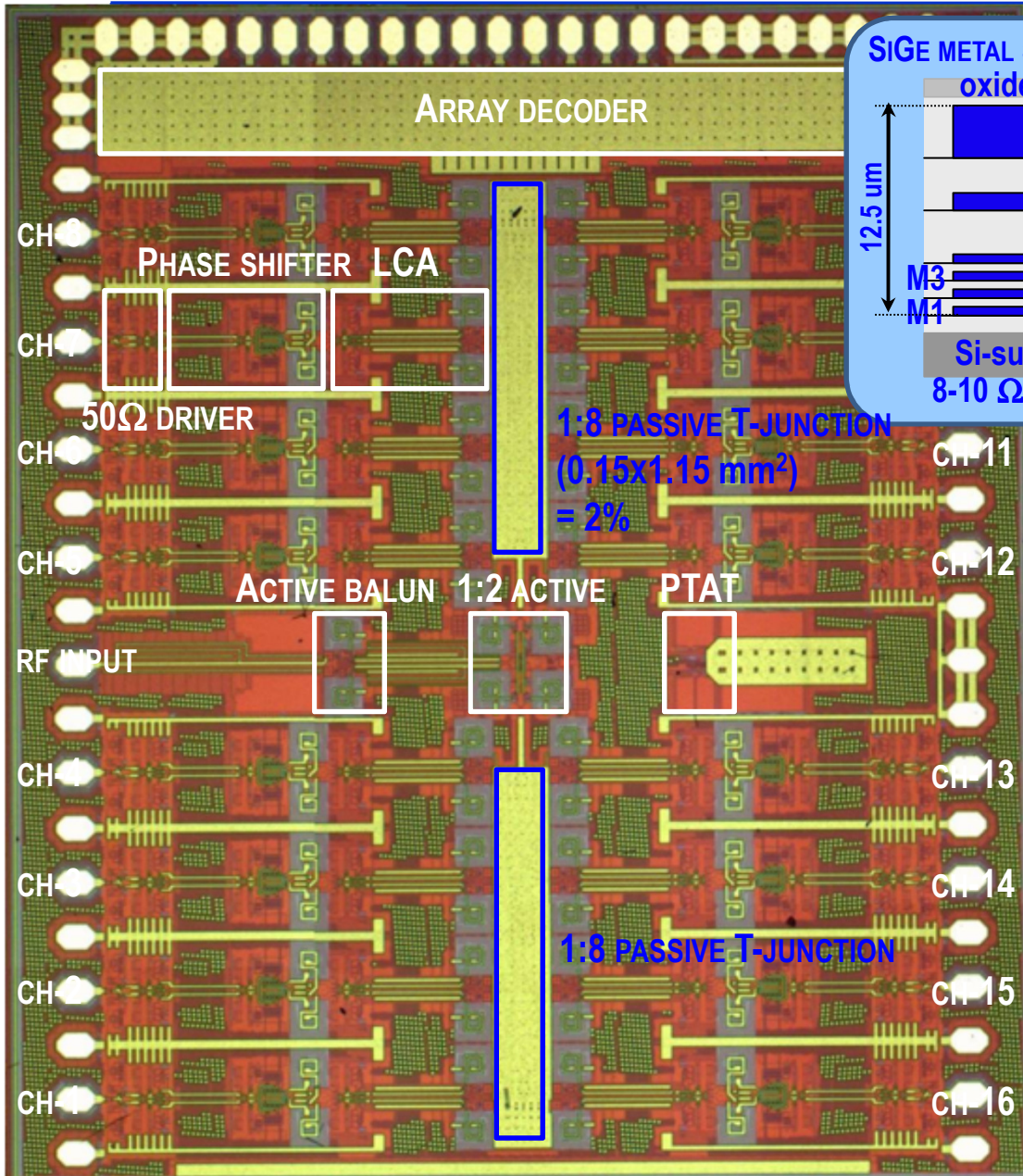16-element Q-band phased-array Tx (44 GHz, 1:8 T-junction)




SHIELDED BROADSIDE-COUPLED DIFF-T-LINE

 


- Perfectly shielded (no coupling btw T-lines)
- Allow compact integration of many diff T-lines


1:8 TEE-JUNCTION DIVIDER

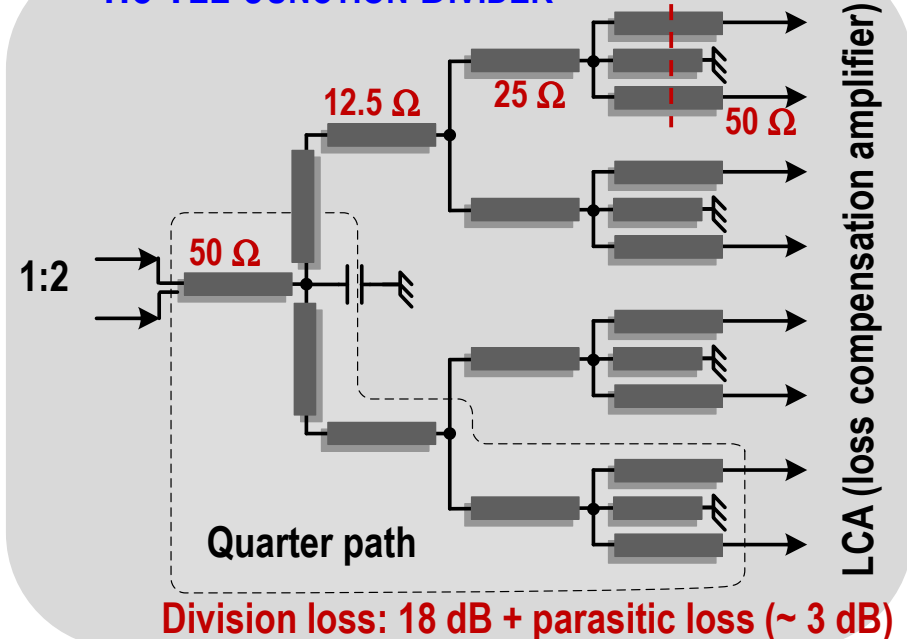

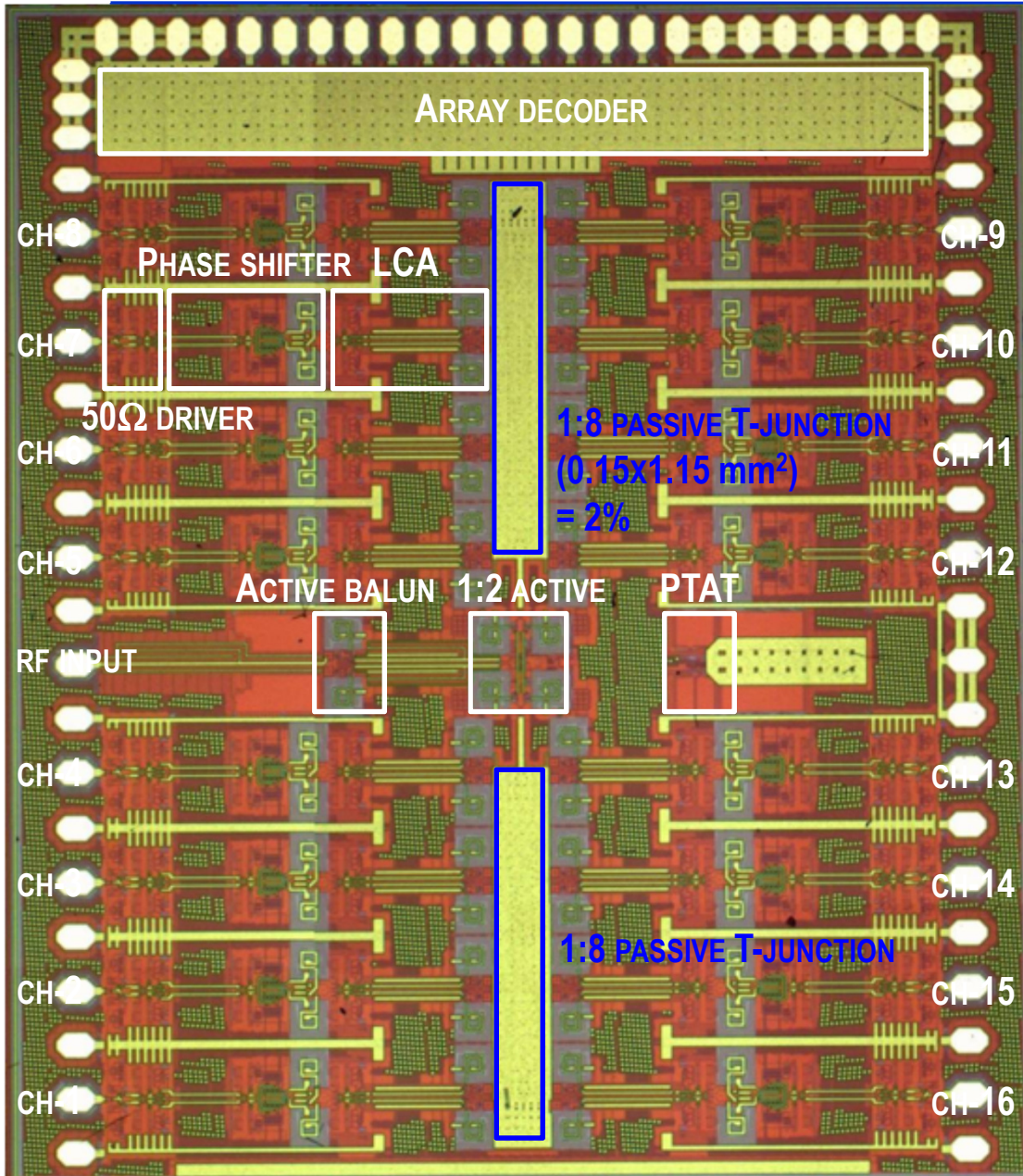16-element Q-band phased-array Tx (44 GHz, coaxial T-line)




SHIELDED BROADSIDE-COUPLED DIFF-T-LINE

 


- Perfectly shielded (no coupling btw T-lines)
- Allow compact integration of many diff T-lines

ODD-MODE E-FIELDS

 

EVEN-MODE E-FIELDS

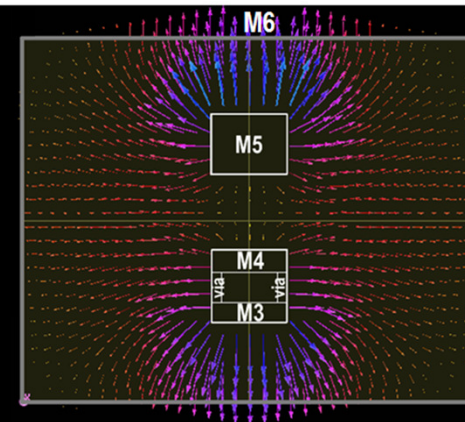

- $W=3\ \mu\text{m}$: odd-mode impedance= $50\ \Omega$ (HFSS sim)
- Most fields (> 95%) are confined btw diff-T lines
- Measured loss: 3 dB / 0.5 mm @45 GHz


16-element Q-band phased-array Tx (44 GHz, measurement)

PARAMETER	RESULTS
Technology	0.18- μm SiGe BiCMOS (Jazz SiGe120, 1P6M)
Supply voltage	5 V (analog), 3.3 V (digital)
Current consumption	$I_{\text{bias}}=720$ mA (44 mA per channel)
Frequency band	Q-band (3-dB BW: 40-45.5 GHz)
Phase resolution	4-bit (accuracy > 5-bit)
Input return loss	< -10 dB @ 36.6-50 GHz
Output return loss	< -10 dB @ 37.6-50 GHz
Power gain (ave)	12.5 dB @ 42.5 GHz
Maximum output power	-2.5 ± 1.5 dBm @ 42.5 GHz
Phase error (RMS)	< 8.8° @ 30-50 GHz
Gain error (RMS)	< 1.3 dB @ 30-50 GHz
Output $P_{1\text{dB}}$	-5 ± 1.5 dBm @ 42.5 GHz
Phase mismatch (RMS)	< 7° @ 30-50 GHz (between all channels)
Amp. mismatch (RMS)	< 1.8 dB @ 30-50 GHz (between all channels)
Isolation (CH-to-CH)	< -30 dB @ 30-50 GHz
Array factor directivity	12 dB (16-element)
Chip area	2.6 x 3.2 mm ²

SINGLE CHANNEL

16-ARRAY

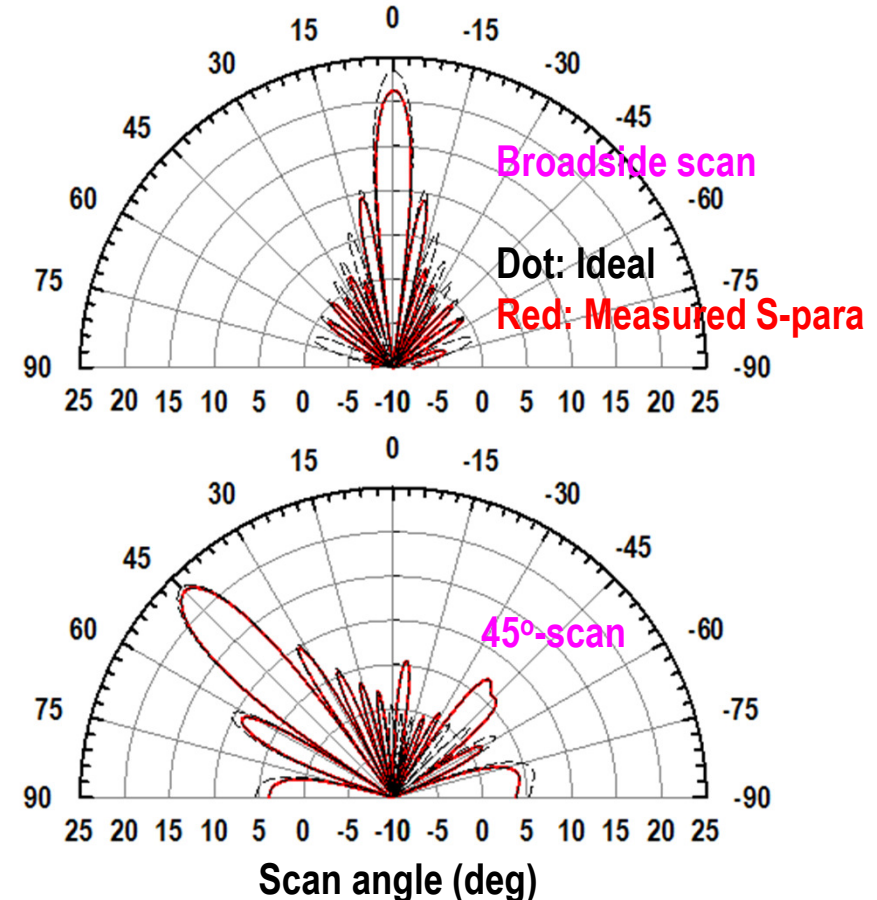BEAM PATTERN BASED ON MEASURED S-PARAMETERS
(16 S-PARA X 16 CHANNELS= 256 S-PARA)




ASSUMPTION


- Isotropic radiator, uniform array spacing, $d=\lambda/2$
- Ideal 45°-scan: $127.3^\circ (= 360^\circ \times d/\lambda \times \sin 45^\circ)$

4-element Q-band phased-array Rx (44 GHz, arch. & chip photo)

PHASED-ARRAY RX BLOCK DIAGRAM

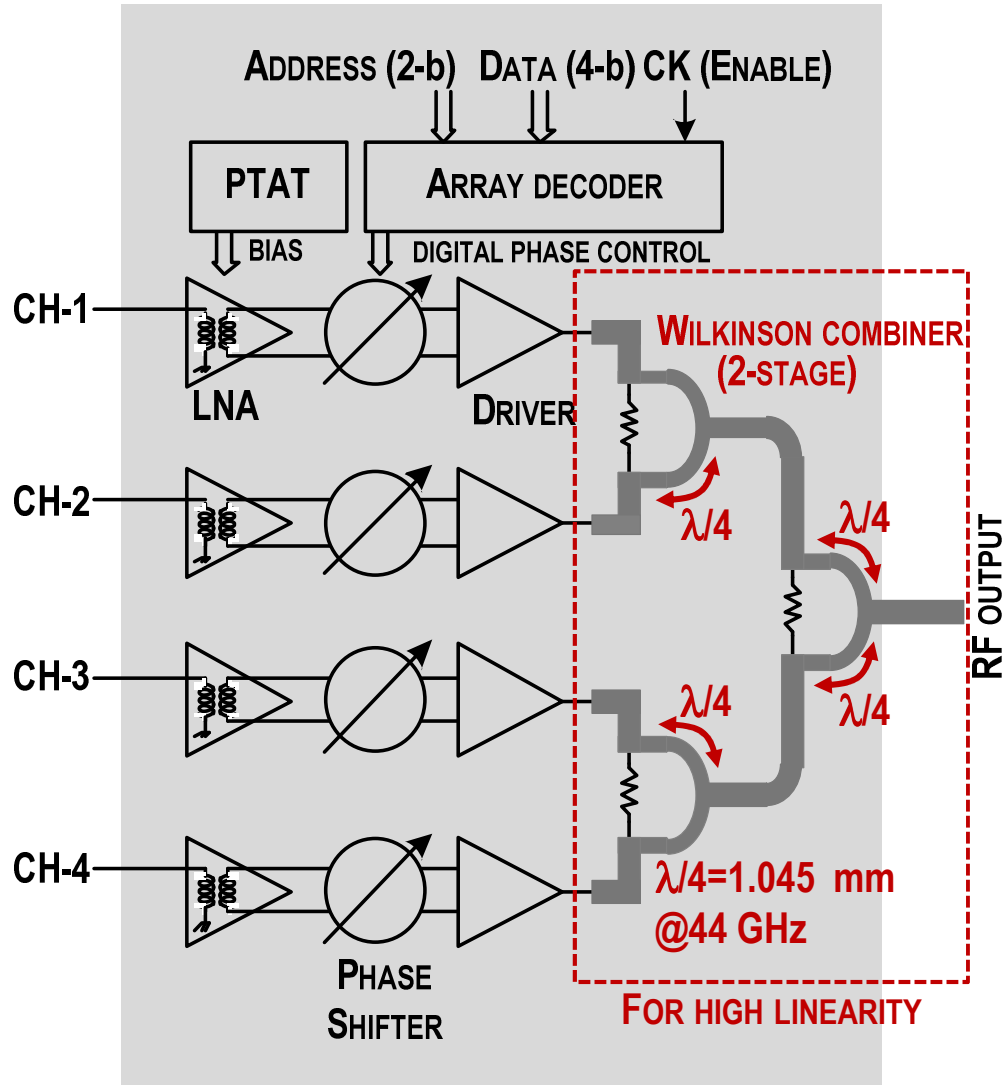


CHIP PHOTOGRAPH

 


SiGe BiCMOS ($f_T=150 \text{ GHz}$), Area=1.4x1.7 mm²

4-element Q-band phased-array Rx (44 GHz, Wilkinson coupler)

WILKINSON COUPLER MEASUREMENTS

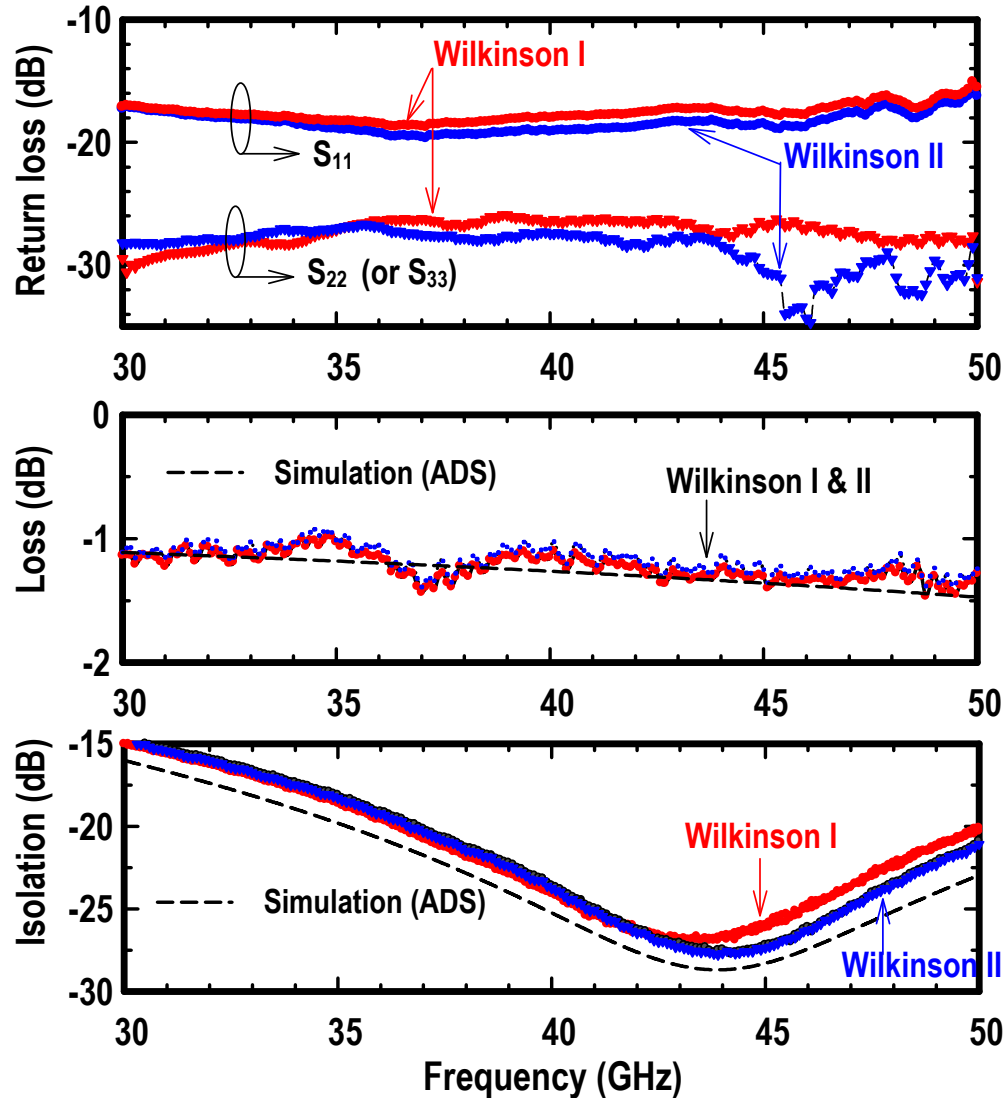


CHIP PHOTOGRAPH

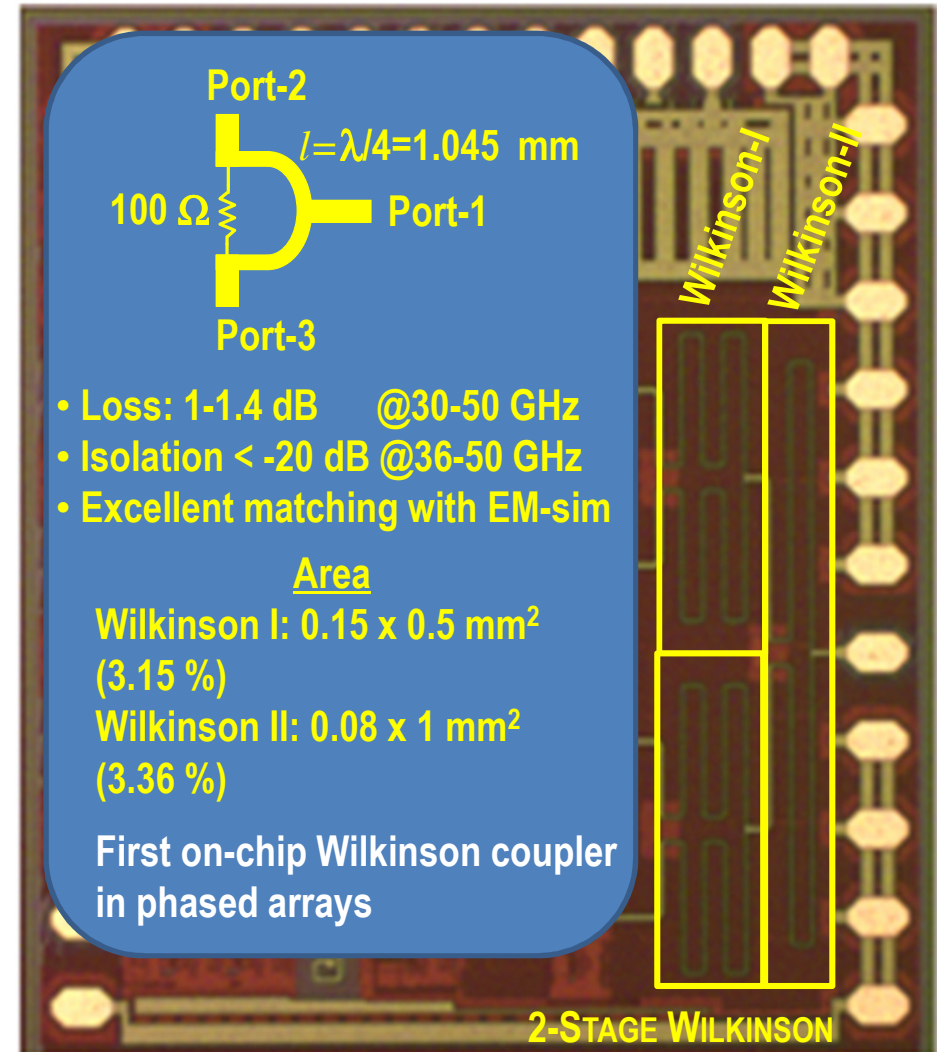

SiGe BiCMOS ($f_T=150 \text{ GHz}$), Area= $1.4 \times 1.7 \text{ mm}^2$

4-element Q-band phased-array Rx (44 GHz, measurement)


PARAMETER	RESULTS
Technology	0.18- μ m SiGe BiCMOS (Jazz SiGe120, 1P6M)
Supply voltage	5 V (analog), 3.3 V (digital)
Current consumption	I_{bias} = 118 mA (29 mA per channel)
Frequency band	Q-band (3-dB BW: 32.3-44 GHz)
Phase resolution	4-bit (accuracy > 5-bit)
Input return loss	< -10 dB @ 40-50 GHz
Output return loss	< -10 dB @ 40-50 GHz
Power gain (ave)	10.4 dB @ 38.5 GHz
NF	12.4 dB @ 38.5 GHz
Phase error (RMS)	< 8.7° @ 30-50 GHz
Gain error (RMS)	< 1.2 dB @ 30-50 GHz
IIP3	-13.8 \pm 1.5 dBm @ 38.5 GHz
Phase mismatch (RMS)	< 2° @ 30-50 GHz (between all channels)
Amp. mismatch (RMS)	< 0.4 dB @ 30-50 GHz (between all channels)
Isolation (CH-to-CH)	< -35 dB @ 30-50 GHz
Array factor directivity	6 dB (4-element)
Chip area	1.4 x 1.7 mm ²

 



Ref: K.-J. Koh *et al*, "A Q-Band Four-Element Phased-Array Front-End Receiver with Integrated Wilkinson Power Combiners in 0.18- μ m SiGe BiCMOS Technology", IEEE Trans. On MTT, Sept 2008

Outline

 - Introduction
 - Discrete phased array: example
- Phase shifter design
 - Active phase shifter
 - Some comparisons with passive one
- Phased array designs
 - X-band receiver
 - Q-band transmitter & receiver
 - **W-band & beyond**
- Conclusion



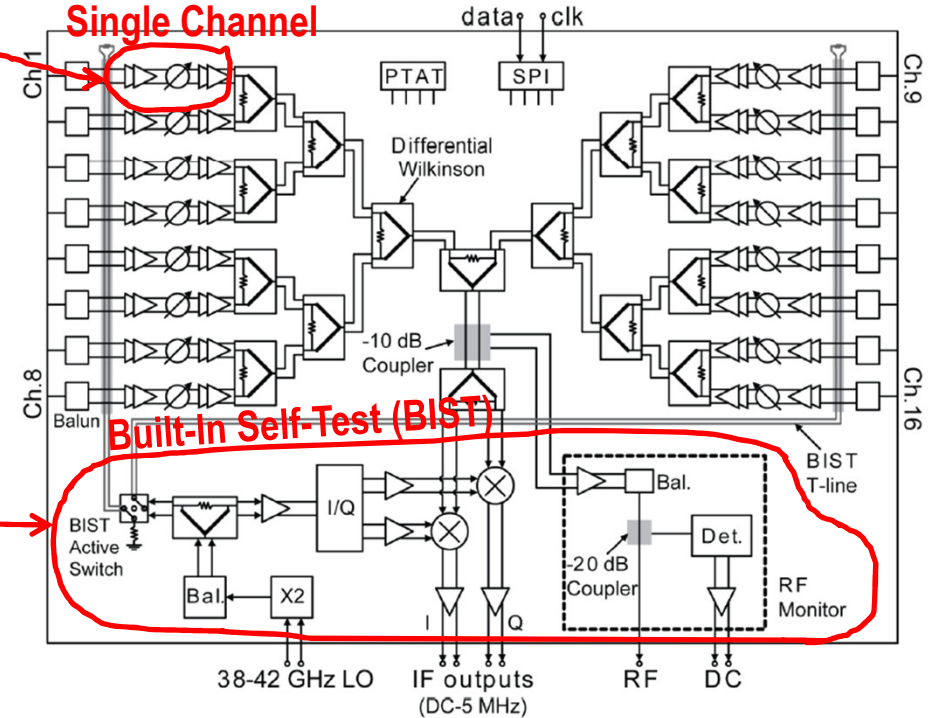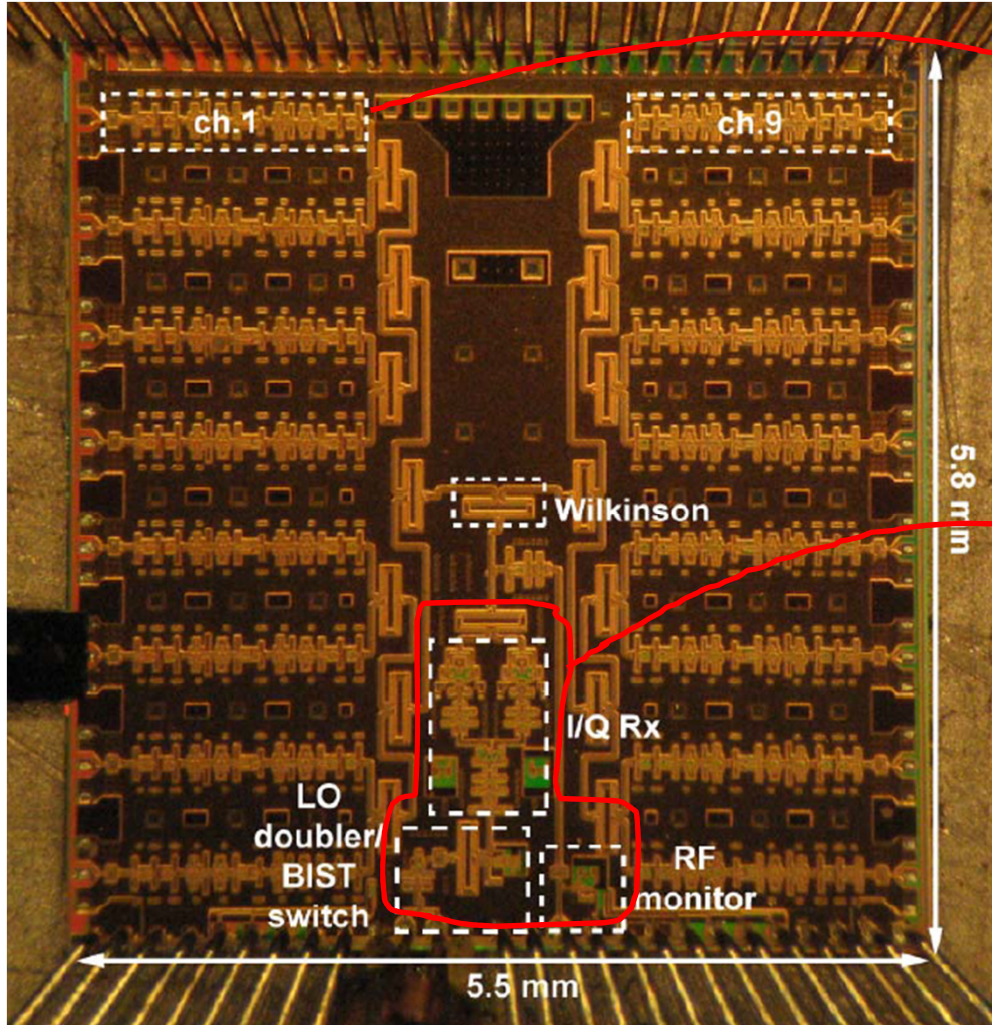16-element W-band phased-array Rx (77-84 GHz)




- Automotive radar applications
- All-RF architecture with 4-stage Wilkinsons
- BIST saves time & cost in measurements
- DC power: $I_{Bias} = 30$ mA/channel, $V_{DD} = 2.1$ V
- Gain: 11-16.5 dB @77-83 GHz
- Phase error (rms): $< 11^\circ$ @77-83 GHz
- Gain error (rms): < 0.9 dB @77-83 GHz
- NF: 12 – 13.5 dB @77-83 GHz
- P1dB: -21 dBm @77GHz, -25 dBm @83 GHz


This work is based on passive phase shifter which works fine at W-band due to high-Q & small size inductors (*more results coming soon from UCSD*).

Conclusions

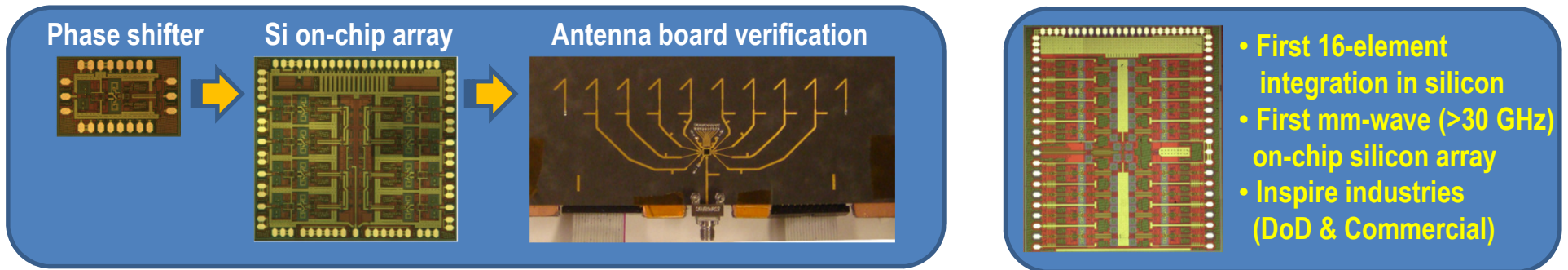- ❑ Provide a low-cost phased array solution for RF and mm-wave defense & commercial applications.
- ❑ First implementation of *All-RF (RF-scanning)* Si phased array IC including system-level demonstration.




 - ❑ Successful technology transfers to DoD industries (Boeing, Lockheed Martin, Raytheon, Teledyne, NG).



Conclusions

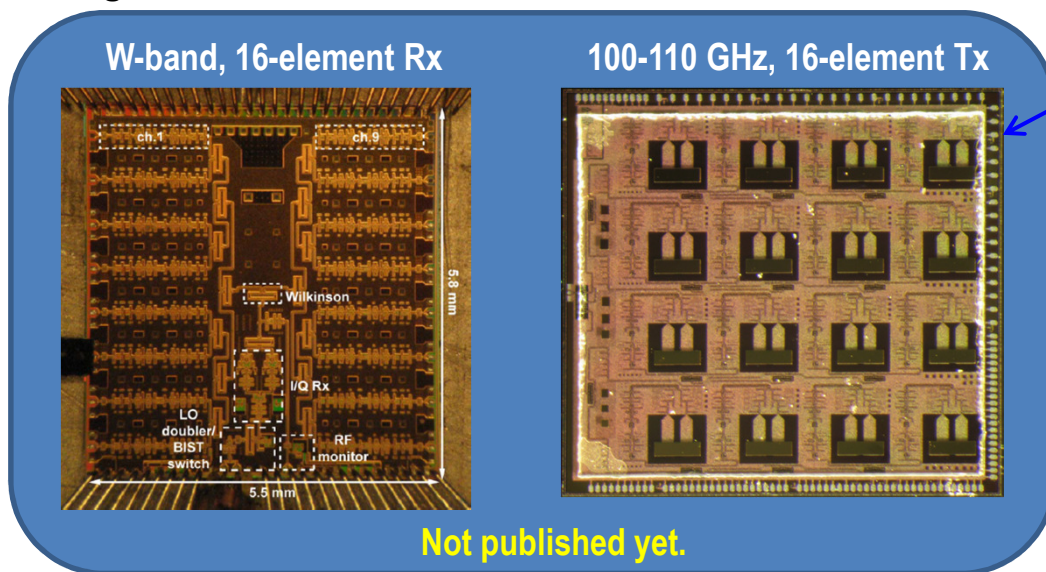- ❑ **All-RF Designs** can be extended further for W-band and beyond > 100 GHz ranges for radar and high data rate mm-wave comm.





This chip integrates 16 Quartz antennas on top of silicon chip (Not presented here, but more results coming from Prof. Rebeiz's group at UCSD) !

- ❑ Now, **All-RF** phased-array architecture becomes industry standard in integrated phased array designs (IBM, MTK, Intel ... all use the **All-RF** based phased array architecture).

Acknowledgement: Most of the works have been supported by DARPA programs. The X- & Q-band phased-arrays were developed as a part of Ph.D study at UCSD under supervision of Prof. Rebeiz. The W-band phased-array receiver was supported by Toyota and developed mainly by S.-Y. Kim, Ph.D student at UCSD Prof. Rebeiz's group. Also, I would like to thank Tower Jazz Semiconductor Corp. for chip fabrications.

  Errors considerations in the active phase shifter (supplementary)



- ❑ Amp (I) and Amp(Q) can be laid out with a good matching.
- ❑ Major error source of output phase will be I/Q network errors (I/Q amp. error, and phase error).
- ❑ Output phase error (Θ_{error}) is a function of combination of I/Q amp. error and phase error.

Ex) For 4-bit accuracy, min phase resolution, $\Delta\theta = 22.5^\circ \rightarrow \Theta_{error}$ should be less than $\Delta\theta/2 = 11.25^\circ$. Therefore, if I/Q amplitude error is 1dB, then I/Q phase error should be within $\sim \pm 10^\circ$ range.

Details of analysis is presented in Kwang-Jin Koh's Ph.D thesis (2008, UCSD).